

Balanced Poly-Phase System

Prepared by
Dr. Mohammad Abdul Mannan
Professor, Department of EEE
American International University – Bangladesh (AIUB)

Poly-phase or Multi-phase Systems

Definition of Poly-phase System:

Circuits or systems in which AC sources operate at the same frequency but different phases are known as **polyphase**.

Poly means **many** and **phases** mean **windings** so that a polyphase generator has many phases or windings.

Definition of Poly-Phase Alternator:

A **polyphase alternator** (synchronous generator) has two or more separate but identical windings (called **phases**) displaced from each other by equal electrical angle and acted upon by the common **uniform magnetic field**. Each winding or phase produces a single alternating voltage of the same magnitude and frequency.

Single-Phase System

The following figure shows a **single phase system**. It has one winding or coil a_1a_2 rotating in anticlockwise or counter-clock wise direction with angular velocity ω in the 2-pole field. Consider the induced emf in the coil is e_{a1a2} .

The equation of the emf induced in the coil is given by:


$$e_{a1a2} = E_m \sin \omega t \quad E_{m1a2} = E_m \cos \phi$$



Four-Phase System

The following figure shows a **four phase system**. It has four windings or coils a_1a_2 , b_1b_2 , c_1c_2 , and d_1d_2 rotating in anticlockwise or counter-clock wise direction with angular velocity ω in the 2-pole field. Consider the induced emfs in these coils are e_{a1a2} , e_{b1b2} , e_{c1c2} , and e_{d1d2} .

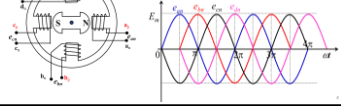The phase difference between two adjacent phases (between a_1a_2 , b_1b_2 , c_1c_2 , between b_1b_2 , c_1c_2 , d_1d_2 , and between d_1d_2 , a_1a_2 , is 90° .)



Four-Phase System Continue.....

The equations of the emfs induced in these coils are given by:

$$e_{a1a2} = E_m \sin \omega t$$

$$e_{b1b2} = E_m \sin(\omega t - 90^\circ)$$

$$e_{c1c2} = E_m \sin(\omega t - 180^\circ) = -E_m \sin \omega t = e_{a1a2}$$

$$e_{d1d2} = E_m \sin(\omega t - 270^\circ) = -E_m(\sin \omega t - 90^\circ) = e_{b1b2}$$


The equations of the emfs in phasor form are given by:

$$E_{a1a2} = E_m \angle 0^\circ$$

$$E_{b1b2} = E_m \angle -90^\circ$$

$$E_{c1c2} = E_m \angle -180^\circ = -E_m \angle 0^\circ = E_{a1a2}$$
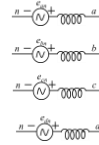
$$E_{d1d2} = E_m \angle -270^\circ = -E_m \angle -90^\circ = E_{b1b2}$$



Two-Phase System

The following figure shows a **two phase system**. It has two windings or coils a_1a_2 and b_1b_2 rotating in anticlockwise or counter-clock wise direction with angular velocity ω in the 2-pole field. Consider the induced emfs in these coils are e_{a1a2} and e_{b1b2} .

The phase difference between two adjacent phases (between a_1a_2 , b_1b_2 and between b_1b_2 , a_1a_2 , is 90° .)


The equations of the emfs induced in these coils are given by:

$$e_{a1a2} = E_m \sin \omega t$$

$$E_{m1a2} = E_m \cos \phi$$

$$e_{b1b2} = E_m \sin(\omega t - 90^\circ)$$


$$E_{b1b2} = E_m \angle -90^\circ$$

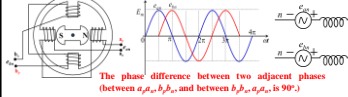

Three-Phase System

The following figure shows a **three phase system**. It has three windings or coils a_1a_2 , b_1b_2 , and c_1c_2 rotating in anticlockwise or counter-clock wise direction with angular velocity ω in the 2-pole field. Consider the induced emfs in these coils are e_{a1a2} , e_{b1b2} , and e_{c1c2} .

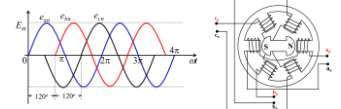The phase difference between two adjacent phases (between a_1a_2 , b_1b_2 , between b_1b_2 , c_1c_2 , and between c_1c_2 , a_1a_2 , is 120° .)



Three-Phase System Continue.....

The equations of the emfs induced in these coils are given by:

$$e_{a1a2} = E_m \sin \omega t$$

$$e_{b1b2} = E_m \sin(\omega t - 120^\circ)$$

$$e_{c1c2} = E_m \sin(\omega t - 240^\circ) = E_m \sin(\omega t + 120^\circ)$$

The equations of the emfs in phasor form are given by:

$$E_{a1a2} = E_m \angle 0^\circ$$

$$E_{b1b2} = E_m \angle -120^\circ$$

$$E_{c1c2} = E_m \angle -240^\circ = E_m \angle 120^\circ$$



Phase Displacement Between Two Adjacent Phases or Windings

The electrical displacement between the windings is determined by the number of phases or windings.

For **other polyphase** systems (e.g. three-phase, four-phase, six-phase) the electrical displacement between different phases or windings can be calculated by:

$$\theta_p = \frac{360^\circ}{n} \quad \text{Where, } n \text{ is the number of phases.}$$

For two phase $n=2$ but $\theta_p = 90^\circ$ This is an exceptional case.

For three phase $n=3$ thus

$$\theta_p = \frac{360^\circ}{3} = \frac{360^\circ}{3} = 120^\circ$$

For four phase $n=4$ thus


$$\theta_p = \frac{360^\circ}{4} = \frac{360^\circ}{4} = 90^\circ$$

For five phase $n=5$ thus

$$\theta_p = \frac{360^\circ}{5} = \frac{360^\circ}{5} = 72^\circ$$

For six phase $n=6$ thus

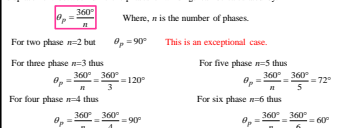
$$\theta_p = \frac{360^\circ}{6} = \frac{360^\circ}{6} = 60^\circ$$



Phase Order or Phase Sequence

The order or sequence in which the voltages in three phases reach their maximum positive values is called **phase order** or **phase sequence**.

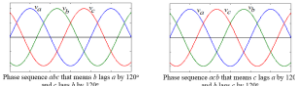The phase sequence is important in determining direction of rotation of ac motors, parallel operation of alternators etc.




Phase sequence abc that means b lags a by 120° and c lags b by 120°.

Phase sequence acb that means c lags a by 120° and b lags c by 120°.

Three phase system has mainly two basic phase order or phase sequence:

abc sequence same as **acb** sequence or **cab** sequence
acb sequence same as **abc** sequence or **bac** sequence

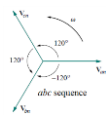Phase Order or Phase Sequence Continue.....




$$\begin{aligned} e_{an} &= E_m \sin \omega t \\ e_{bn} &= E_m \sin(\omega t - 120^\circ) \\ e_{cn} &= E_m \sin(\omega t - 240^\circ) = E_m \sin(\omega t + 120^\circ) \\ E_{an} &= E_m \angle 0^\circ = E_m (1 - j0) \\ E_{bn} &= E_m \angle -120^\circ = E_m (-0.5 - j0.866) \\ E_{cn} &= E_m \angle -240^\circ = E_m \angle 120^\circ = E_m (-0.5 + j0.866) \end{aligned}$$

abc sequence: the end of phase b lags that of a by 120°. Also, the end of phase c lags that of phase b by 120° that means the end of phase c lags that of phase a by 240°.

$$E_{an} = E_m \angle 0^\circ \quad E_{bn} = E_m \angle -120^\circ \quad E_{cn} = E_m \angle 120^\circ$$

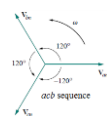Phase Order or Phase Sequence Continue.....



$$\begin{aligned} e_{an} &= E_m \sin \omega t \\ e_{bn} &= E_m \sin(\omega t - 120^\circ) \\ e_{cn} &= E_m \sin(\omega t - 240^\circ) = E_m \sin(\omega t + 120^\circ) \\ E_{an} &= E_m \angle 0^\circ = E_m (1 - j0) \\ E_{bn} &= E_m \angle -120^\circ = E_m (-0.5 - j0.866) \\ E_{cn} &= E_m \angle -240^\circ = E_m \angle 120^\circ = E_m (-0.5 + j0.866) \end{aligned}$$

acb sequence: the end of phase c lags that of a by 120°. Also, the end of phase b lags that of phase c by 120° that means the end of phase b lags that of phase a by 240°.

$$E_{an} = E_m \angle 0^\circ \quad E_{bn} = E_m \angle 120^\circ \quad E_{cn} = E_m \angle -120^\circ$$

Example 9.1

Determine the phase sequence of the set of voltages: $v_{an} = \sqrt{2} \cdot 200 \sin(\omega t + 10^\circ)$, $v_{bn} = \sqrt{2} \cdot 200 \sin(\omega t - 230^\circ)$, and $v_{cn} = \sqrt{2} \cdot 200 \sin(\omega t - 110^\circ)$

Solution: The voltages can be expressed in phasor form as:


$$V_{an} = 200 \angle 10^\circ \text{ V} \quad V_{bn} = 200 \angle -230^\circ \text{ V} \quad V_{cn} = 200 \angle -110^\circ \text{ V}$$

We note that V_{cn} lags V_{an} by 120° and V_{bn} lags V_{cn} by 120°; hence we have acb sequence.

Double-Subscript Notation of Voltage

When a voltage is represented by a double subscript (such as V_{ab}) its first letter (such as a) represents the **positive terminal** and second letter (such as b) represents the **negative terminal**.

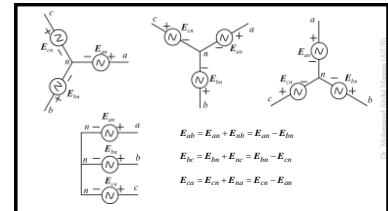
$$\begin{aligned} V_{ab} &= V_{ba} + V_{bc} = V_{ac} - V_{cb} \\ V_{bd} &= V_{bc} + V_{cd} = V_{bd} - V_{db} \\ V_{ad} &= V_{ab} + V_{bd} = V_{ad} - V_{da} \end{aligned}$$



Double-Subscript Notation of Current

When a current is represented by a double subscript (such as I_{ab}) its first letter (such as a) represents the **entering terminal** and second letter (such as b) represents the **leaving terminal**.

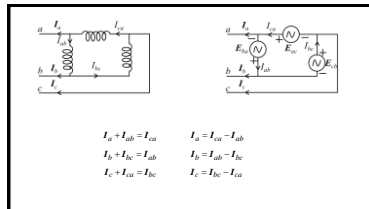
$$\begin{aligned} I_{ab} &= I_{ba} + I_{bc} = I_{ba} - I_{cb} \\ I_{bc} &= I_{cb} - I_{ba} \\ I_{ca} &= I_{cb} - I_{ba} \\ I_{ab} &= I_{ba} - I_{cb} \\ I_{bc} &= I_{cb} - I_{ba} \\ I_{ca} &= I_{cb} - I_{ba} \end{aligned}$$




Connections of Poly-Phase



Connection of poly-phase systems are two types:
 1. Star Connection
 2. Mesh Connection

Star Connection

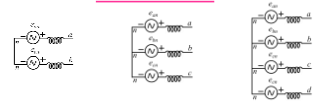


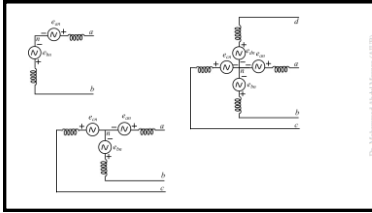

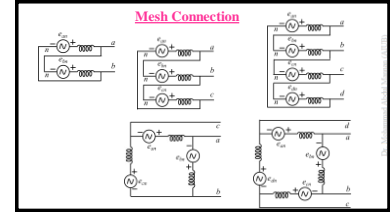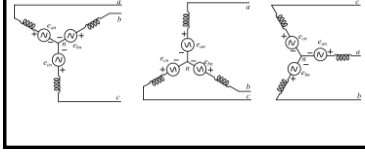The three-phase star connection looks like a Y that's why three-phase star connection is also called **wye-connection** or **Y-connection**.



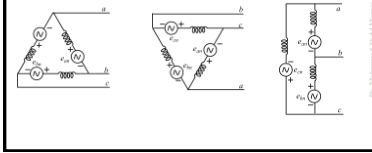The three-phase mesh connection looks like a delta (Δ) that's why three-phase star connection is also called **delta-connection** or **Δ -connection**.




Line Voltage of Star Connection

Let, a four-phase star connected source is connected with a load.


Phase voltages: $E_{a0}, E_{b0}, E_{c0},$ and E_{d0} . **Phase currents:** $I_{a0}, I_{b0}, I_{c0},$ and I_{d0} .

Line voltages: $E_{ab}, E_{bc}, E_{cd},$ and E_{da} .

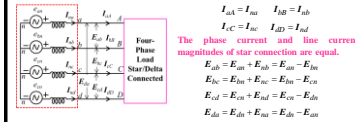Line currents: $I_{ab}, I_{bc}, I_{cd},$ and I_{da} .



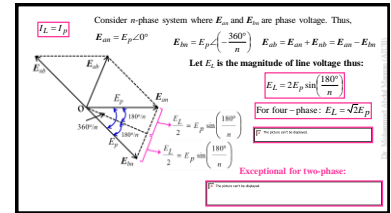The phase voltage and line voltage magnitudes of star connection are not equal.




Line Current of Mesh Connection

Let, a four-phase mesh connected source is connected with a load.



Phase voltages: $E_{a0}, E_{b0}, E_{c0},$ and E_{d0} . **Phase currents:** $I_{a0}, I_{b0}, I_{c0},$ and I_{d0} .

Line voltages: $E_{ab}, E_{bc}, E_{cd},$ and E_{da} .

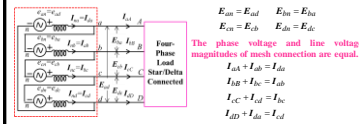Line currents: $I_{ab}, I_{bc}, I_{cd},$ and I_{da} .



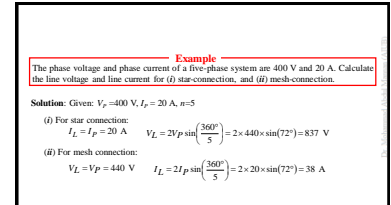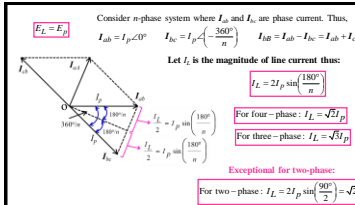The phase voltage and line voltage magnitudes of star connection are not equal.



Home Work 9.1

Problem 9.1.1: Determine the phase sequence for the following sets of three-phase voltages: (a) $e_{an} = 25\sin(\omega t - 50^\circ)$ (b) $e_{an} = 20\sin(\omega t + 40^\circ)$
 $e_{bn} = 25\sin(\omega t + 70^\circ)$ $e_{bn} = 20\sin(\omega t - 80^\circ)$
 $e_{cn} = 25\sin(\omega t - 170^\circ)$ $e_{cn} = 20\sin(\omega t + 160^\circ)$

Problem 9.1.2: The line voltage and line current of a five-phase system are 1500 V and 200 A. Calculate the phase voltage and phase current for (i) star-connection, and (ii) mesh-connection.

Problem 9.1.3: If the phase current is 100 A and phase voltage is 330 V for a balanced four-phase system, find the magnitude of the line voltage and the line current for (i) the star-connection, and (ii) the mesh-connection.

Problem 9.1.4: If the line current is 120 A and line voltage is 440 V for a balanced five-phase system, find the magnitude of the phase voltage and the phase current for (i) the star-connection, and (ii) the mesh-connection.

Three-Phase Star or Y Connection

Phase Voltages: E_{an}, E_{bn}, E_{cn}

Line Voltages: E_{ab}, E_{bc}, E_{ca}

Phase Currents: I_{an}, I_{bn}, I_{cn}

Line Currents: I_{ab}, I_{bc}, I_{ca}

$I_{aA} = I_{an}; I_{bB} = I_{bn}; I_{cC} = I_{cn}$

Line Currents = Phase Currents

$E_{an} = E_p \angle 0^\circ$

$E_{bn} = E_p \angle -120^\circ$


$E_{cn} = E_p \angle -240^\circ = E_p \angle 120^\circ$

$E_{ab} = E_{an} + E_{bn} = E_{an} - E_{bn} = \sqrt{3}E_p \angle 30^\circ$


$E_{bc} = E_{bn} + E_{cn} = E_{bn} - E_{cn} = \sqrt{3}E_p \angle -90^\circ$

$E_{ca} = E_{cn} + E_{an} = E_{cn} - E_{an} = \sqrt{3}E_p \angle -210^\circ$

$E_{ca} = \sqrt{3}E_p \angle 150^\circ$

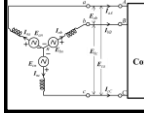

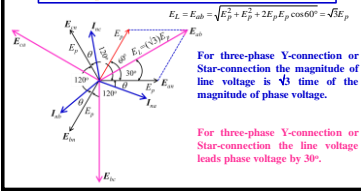Vector Diagram for Three-Phase Star or Y Connected Source



Three-Phase Mesh or Δ Connection

Phase Voltages: E_{ab}, E_{bc}, E_{ca}

Line Voltages: E_{ab}, E_{bc}, E_{ca}

Phase Currents: I_{ab}, I_{bc}, I_{ca}

Line Currents: I_{aA}, I_{bB}, I_{cC}

$E_{ab} = E_{an}; E_{bc} = E_{bn}; E_{ca} = E_{cn}$

Line voltages = Phase Voltages

$I_{ba} = I_p \angle 0^\circ$


$I_{cb} = I_p \angle -120^\circ$

$I_{ac} = I_p \angle -240^\circ = I_p \angle 120^\circ$


$I_{aA} = I_{ba} - I_{ac} = \sqrt{3}I_p \angle -30^\circ$

$I_{bB} = I_{cb} - I_{ba} = \sqrt{3}I_p \angle -150^\circ$

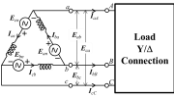$I_{cC} = I_{ac} - I_{cb} = \sqrt{3}I_p \angle -270^\circ = \sqrt{3}I_p \angle 90^\circ$



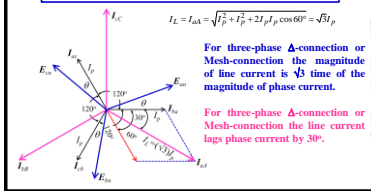Vector Diagram for Three-Phase Mesh or Δ Connected Source



Balanced Source System

A set of three phase quantities (phase voltages or phase currents or line voltages or line currents), all the same frequency with equal peak (and hence equal rms) values and shifted (or displaced) successively by 120° is defined as a **Balanced Three-Phase Quantity**.

$E_{an} = E_{bn} = E_{cn} = E_p$

$I_{an} = I_{bn} = I_{cn} = I_p$

$E_{ab} = E_{bc} = E_{ca} = E_L$

$I_{aA} = I_{bB} = I_{cC} = I_L$


$E_{an} + E_{bn} + E_{cn} = 0$

$I_{an} + I_{bn} + I_{cn} = 0$


$E_{ab} + E_{bc} + E_{ca} = 0$

$I_{aA} + I_{bB} + I_{cC} = 0$

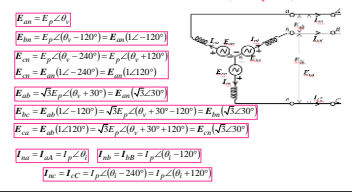
Y-Connected Balanced Source (abc sequence)



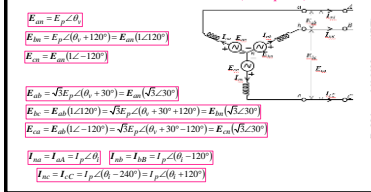Y-Connected Balanced Source (acb sequence)



Example

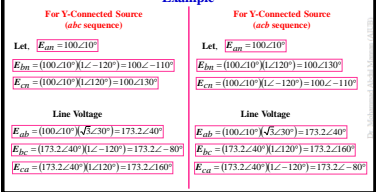

Example

For Y-Connected Source (abc sequence)

Let. $E_{ab} = 260\angle 30^\circ$

$E_{bc} = (260\angle 30^\circ)(\angle -120^\circ) = 260\angle -90^\circ$

$E_{ca} = (260\angle 30^\circ)(\angle 120^\circ) = 260\angle 150^\circ$

Phase Voltage

$E_{an} = (260\angle 30^\circ)\left(\frac{1}{\sqrt{3}}\angle -30^\circ\right) = 150\angle 0^\circ$

$E_{bn} = (150\angle 0^\circ)(\angle -120^\circ) = 150\angle -120^\circ$

$E_{cn} = (150\angle 0^\circ)(\angle 120^\circ) = 150\angle 120^\circ$

For Y-Connected Source (acb sequence)

Let. $E_{ab} = 260\angle 30^\circ$

$E_{bc} = (260\angle 30^\circ)(\angle 120^\circ) = 260\angle 150^\circ$

$E_{ca} = (260\angle 30^\circ)(\angle -120^\circ) = 260\angle -90^\circ$

Phase Voltage

$E_{an} = (260\angle 30^\circ)\left(\frac{1}{\sqrt{3}}\angle -30^\circ\right) = 150\angle 0^\circ$

$E_{bn} = (150\angle 0^\circ)(\angle 120^\circ) = 150\angle 120^\circ$

$E_{cn} = (150\angle 0^\circ)(\angle -120^\circ) = 150\angle -120^\circ$

Δ-Connected Balanced Source (abc sequence)

$I_{ba} = I_p \angle \theta$

$I_{cb} = I_p \angle (\theta - 120^\circ) = I_{ba}(\angle -120^\circ)$

$I_{ac} = I_p \angle (\theta + 120^\circ) = I_{ba}(\angle 120^\circ)$

$I_{ab} = \sqrt{3}I_p \angle (\theta - 30^\circ) = I_{ba}(\sqrt{3}\angle -30^\circ)$

$I_{bc} = I_{ab}(\angle -120^\circ) = \sqrt{3}I_p \angle (\theta + 30^\circ - 120^\circ) = I_{ab}(\sqrt{3}\angle -90^\circ)$

$I_{ca} = I_{ab}(\angle 120^\circ) = \sqrt{3}I_p \angle (\theta - 30^\circ + 120^\circ) = I_{ab}(\sqrt{3}\angle 90^\circ)$

$E_{ab} = E_{ab} = E_p \angle \theta$ $E_{bc} = E_{bc} = E_{ab}(\angle -120^\circ) = E_p \angle (\theta - 120^\circ)$

$E_{ca} = E_{ca} = E_{ab}(\angle 120^\circ) = E_p \angle (\theta + 120^\circ)$

Δ-Connected Balanced Source (acb sequence)

$I_{ba} = I_p \angle \theta$

$I_{cb} = I_p \angle (\theta + 120^\circ) = I_{ba}(\angle 120^\circ)$

$I_{ac} = I_p \angle (\theta - 120^\circ) = I_{ba}(\angle -120^\circ)$

$I_{ab} = \sqrt{3}I_p \angle (\theta - 30^\circ) = I_{ba}(\sqrt{3}\angle -30^\circ)$

$I_{bc} = I_{ab}(\angle 120^\circ) = \sqrt{3}I_p \angle (\theta + 30^\circ + 120^\circ) = I_{ab}(\sqrt{3}\angle 150^\circ)$

$I_{ca} = I_{ab}(\angle -120^\circ) = \sqrt{3}I_p \angle (\theta - 30^\circ - 120^\circ) = I_{ab}(\sqrt{3}\angle -150^\circ)$

$E_{ab} = E_{ab} = E_p \angle \theta$ $E_{bc} = E_{bc} = E_{ab}(\angle 120^\circ) = E_p \angle (\theta + 120^\circ)$

$E_{ca} = E_{ca} = E_{ab}(\angle -120^\circ) = E_p \angle (\theta - 120^\circ)$

Example

For Δ-Connected Source (abc sequence)

Let. $I_{ba} = 10\angle -20^\circ$

$I_{cb} = (10\angle -20^\circ)(\angle -120^\circ) = 10\angle -140^\circ$

$I_{ac} = (10\angle -20^\circ)(\angle 120^\circ) = 10\angle 100^\circ$

Line Current

$I_{aA} = (10\angle -20^\circ)\left(\sqrt{3}\angle -30^\circ\right) = 17.3\angle -50^\circ$

$I_{bB} = (17.3\angle -50^\circ)(\angle -120^\circ) = 17.3\angle -170^\circ$

$I_{cC} = (17.3\angle -50^\circ)(\angle 120^\circ) = 17.3\angle 70^\circ$

For Δ-Connected Source (acb sequence)

Let. $I_{ba} = 10\angle -20^\circ$

$I_{cb} = (10\angle -20^\circ)(\angle 120^\circ) = 10\angle 100^\circ$

$I_{ac} = (10\angle -20^\circ)(\angle -120^\circ) = 10\angle -140^\circ$

Line Current

$I_{aA} = (10\angle -20^\circ)\left(\sqrt{3}\angle 30^\circ\right) = 17.3\angle 10^\circ$

$I_{bB} = (17.3\angle 10^\circ)(\angle 120^\circ) = 17.3\angle 130^\circ$

$I_{cC} = (17.3\angle 10^\circ)(\angle -120^\circ) = 17.3\angle -110^\circ$

Example

For Δ-Connected Source (abc sequence)

Let. $I_{aA} = 260\angle -30^\circ$

$I_{bB} = (260\angle -30^\circ)(\angle -120^\circ) = 260\angle -150^\circ$

$I_{cC} = (260\angle -30^\circ)(\angle 120^\circ) = 260\angle 90^\circ$

Phase Current

$I_{ba} = (260\angle -30^\circ)\left(\frac{1}{\sqrt{3}}\angle 30^\circ\right) = 150\angle 0^\circ$

$I_{cb} = (150\angle 0^\circ)(\angle -120^\circ) = 150\angle -120^\circ$

$I_{ac} = (150\angle 0^\circ)(\angle 120^\circ) = 150\angle 120^\circ$

For Δ-Connected Source (acb sequence)

Let. $I_{aA} = 260\angle -30^\circ$

$I_{bB} = (260\angle -30^\circ)(\angle 120^\circ) = 260\angle 90^\circ$

$I_{cC} = (260\angle -30^\circ)(\angle -120^\circ) = 260\angle -150^\circ$

Phase Current

$I_{ba} = (260\angle -30^\circ)\left(\frac{1}{\sqrt{3}}\angle -30^\circ\right) = 150\angle -60^\circ$

$I_{cb} = (150\angle -60^\circ)(\angle 120^\circ) = 150\angle 60^\circ$

$I_{ac} = (150\angle -60^\circ)(\angle -120^\circ) = 150\angle -180^\circ$

Conversion from Y-Connected Source to Δ-Connected Balanced Source

$E_{ab} = E_{an}(\sqrt{3}\angle 30^\circ)$

$E_{bc} = E_{an}(\angle 120^\circ) = E_{ab}(\sqrt{3}\angle 30^\circ)$

$E_{ca} = E_{an}(\angle -120^\circ) = E_{ab}(\sqrt{3}\angle 30^\circ)$

Example

The following Y-connected source convert to Δ-Connected Source

Here, for Y-connected source

$E_{an} = 100\angle 0^\circ$

$E_{bn} = 100\angle -120^\circ$

$E_{cn} = 100\angle 120^\circ$

Here, for Δ-connected source

$E_{ab} = (100\angle 0^\circ)\left(\sqrt{3}\angle 30^\circ\right) = 173.2\angle 30^\circ$

$E_{bc} = (173.2\angle 30^\circ)(\angle -120^\circ) = 173.2\angle -90^\circ$

$E_{ca} = (173.2\angle 30^\circ)(\angle 120^\circ) = 173.2\angle 150^\circ$

Example

The following Δ-connected source convert to Y-Connected Source

Here, for Δ-connected source

$E_{ab} = 260\angle 0^\circ$

$E_{bc} = 260\angle -120^\circ$

$E_{ca} = 260\angle 120^\circ$

Here, for Y-connected source

$E_{an} = (260\angle 0^\circ)\left(\frac{1}{\sqrt{3}}\angle -30^\circ\right) = 150\angle -30^\circ$

$E_{bn} = (150\angle -30^\circ)(\angle -120^\circ) = 150\angle -150^\circ$

$E_{cn} = (150\angle -30^\circ)(\angle 120^\circ) = 150\angle 90^\circ$

Conversion from Δ-Connected Source to Y-Connected Balanced Source

$E_{an} = E_{ab}\left(\frac{1}{\sqrt{3}}\angle -30^\circ\right)$

$E_{bn} = E_{ab}(\angle -120^\circ) = E_{an}\left(\frac{1}{\sqrt{3}}\angle -30^\circ\right)$

$E_{cn} = E_{ab}(\angle 120^\circ) = E_{an}\left(\frac{1}{\sqrt{3}}\angle -30^\circ\right)$

Balanced Load

A set of three phase load impedances, all the same value is defined as a **Balanced Three-Phase load**.

Y-Connected load



For Balanced load

$$Z_A = Z_B = Z_C = Z_Y$$

$$Z_{AB} = Z_{BC} = Z_{CA} = Z_{\Delta}$$

$$Z_Y = \frac{Z_{\Delta}}{3}$$


$$Z_{\Delta} = 3Z_Y$$

Δ -Connected load



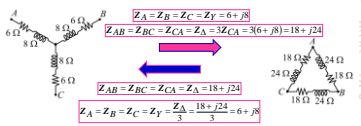Example

Conversion from Y-connected load convert to Δ -Connected load and vice versa



Three-Phase Power

Let, the current and voltage of a three-phase system are:

$$i_{an} = I_m \sin \omega t; \quad i_{bn} = I_m \sin(\omega t - 120^\circ); \quad i_{cn} = I_m \sin(\omega t + 120^\circ)$$

$$v_{an} = V_m \sin(\omega t + \theta); \quad v_{bn} = V_m \sin(\omega t + \theta - 120^\circ); \quad v_{cn} = V_m \sin(\omega t + \theta + 120^\circ)$$

The power of each individual phase are given by:

$$p_a(t) = v_{an} i_{an}; \quad p_b(t) = v_{bn} i_{bn}; \quad p_c(t) = v_{cn} i_{cn}$$

The total three-phase power is given by:

$$p_{3\phi}(t) = p_a(t) + p_b(t) + p_c(t) = v_{an} i_{an} + v_{bn} i_{bn} + v_{cn} i_{cn}$$

The total three-phase power for a balanced system is given by:

$$P_{3\phi}(t) = 3p_a(t) = 3p_b(t) = 3p_c(t) = 3v_{an} i_{an} = 3v_{an} i_{m} \cos \theta$$

$$P_{3\phi}(t) = \frac{3}{2} V_m I_m \cos \theta$$

Let, V_p is the rms value of phase voltage and I_p is the rms value of phase current that means:

$$V_p = \frac{V_m}{\sqrt{2}}; \quad I_p = \frac{I_m}{\sqrt{2}}$$

Thus, the total three-phase power for a balanced system is given by:

$$P_{3\phi}(t) = 3V_p I_p \cos \theta$$

The power of a single phase system is given by:

$$p_a(t) = P[1 - \cos 2\omega t] + Q \sin 2\omega t$$

The single-phase power changes with respect to the time, so the single phase machine vibrates and makes noise. On the other hand, the three-phase machine does not depend on time so it is constant and the three-phase machine is not vibrated and does not make noise.

Let, V_L is the rms value of line voltage and I_L is the rms value of line current.

For Y-connection

$$V_L = \sqrt{3} V_p; \quad I_L = I_p$$

For Δ -connection

$$I_L = I_p; \quad V_L = \sqrt{3} V_p$$

$$P = 3V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$Q = 3V_p I_p \sin \theta = \sqrt{3} V_L I_L \sin \theta$$

$$S = 3V_p I_p = \sqrt{3} V_L I_L$$



$$pf = \cos \theta = \frac{P}{S}$$

$$pf = \sin \theta = \frac{Q}{S}$$

Example (Y \rightarrow Y)

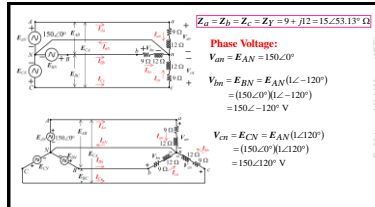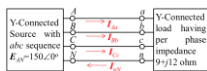Example (Y \rightarrow Y)

A three-phase Y-connected balanced source with abc sequence is connected with a Y-connected balanced load having the per phase impedance $9 + j12 \, \Omega$. The neutrals of both source and load are connected. The phase voltage of source is given by $E_{an} = 150 \angle 0^\circ \text{ V}$. Calculate (i) the phase voltages (V_{an}, V_{bn}, V_{cn}), (ii) the line voltages (E_{ab}, E_{bc}, E_{ca}), (iii) the phase currents (I_{an}, I_{bn}, I_{cn}), (iv) the line currents (I_{La}, I_{Lb}, I_{Lc}), (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.



Line Voltage:

$$E_{AB} = E_{AN} - E_{BN} = E_{AN}(\sqrt{3} \angle 30^\circ) - (150 \angle 0^\circ)(\sqrt{3} \angle 30^\circ) = 260 \angle 30^\circ \text{ V}$$

$$E_{BC} = E_{BN} - E_{CN} = E_{BN}(\sqrt{3} \angle 30^\circ) - E_{AN} \angle -120^\circ = 260 \angle -90^\circ \text{ V}$$

$$E_{CA} = E_{CN} - E_{AN} = E_{CN}(\sqrt{3} \angle 30^\circ) - E_{AB} \angle 120^\circ = 260 \angle 150^\circ \text{ V}$$

For Y connection: Phase Current = Line Current

$$I_{an} = I_{La} = \frac{V_{an}}{Z_{\Delta}} = \frac{150 \angle 0^\circ}{15 \angle 53.13^\circ} = 10 \angle -53.13^\circ \text{ A}$$

$$I_{bn} = I_{Lb} = \frac{V_{bn}}{Z_{\Delta}} = \frac{150 \angle -120^\circ}{15 \angle 53.13^\circ} = 10 \angle -173.13^\circ \text{ A}$$

$$I_{cn} = I_{Lc} = \frac{V_{cn}}{Z_{\Delta}} = \frac{150 \angle 120^\circ}{15 \angle 53.13^\circ} = 10 \angle 66.87^\circ \text{ A}$$

Power factor and Reactive factor:

$$\theta = \theta_v - \theta_i = 0^\circ - (-53.13^\circ) = 53.13^\circ$$

$$pf = \cos \theta = \cos(53.13^\circ) = 0.6$$

$$rf = \sin \theta = \sin(53.13^\circ) = 0.8$$

Apparent Power, Real Power and Reactive Power

$$V_L = 260 \text{ V}; \quad I_L = 10 \text{ A}$$



$$S = \sqrt{3} V_L I_L = \sqrt{3} \times 260 \times 10 = 4503.3 \text{ VA}$$

$$P = \sqrt{3} V_L I_L \cos \theta = S \cos \theta = 4503.3 \times 0.6 = 2702 \text{ W}$$

$$Q = \sqrt{3} V_L I_L \sin \theta = S \sin \theta = 4503.3 \times 0.8 = 3602.7 \text{ VAR}$$

Example (Y→Δ)**Example (Y→Δ)**


A three-phase Y-connected balanced source is connected with a Δ-connected balanced load having the per phase impedance $9+j12 \Omega$. The phase voltage of source is given by $E_{an}=150\angle 0^\circ$ V. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.

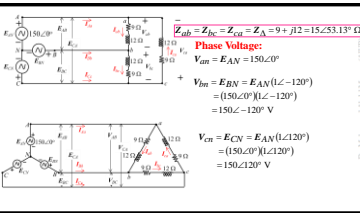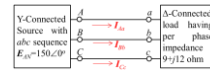**Line Voltage:**

$$E_{AB} = E_{AN} - E_{BN} = E_{AN}(\sqrt{3}\angle 30^\circ) = (150\angle 0^\circ)(\sqrt{3}\angle 30^\circ) = 260\angle 30^\circ \text{ V}$$

$$E_{BC} = E_{BN} - E_{CN} = E_{BN}(\sqrt{3}\angle 30^\circ) = E_{AB}(\angle -90^\circ) = 260\angle -90^\circ \text{ V}$$

$$E_{CA} = E_{CN} - E_{AN} = E_{CN}(\sqrt{3}\angle 30^\circ) = E_{AB}(\angle 120^\circ) = 260\angle 150^\circ \text{ V}$$

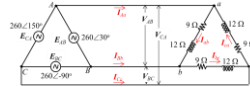Converts Y-connected source to Δ-connected source:**Phase Current:**

$$I_{ab} = \frac{E_{AB}}{Z_{ab}} = \frac{260\angle 30^\circ}{15\angle 53.13^\circ} = 17.33\angle -23.13^\circ \text{ A}$$

$$I_{bc} = \frac{E_{BC}}{Z_{bc}} = I_{ab}(\angle -120^\circ) = 17.33\angle -143.13^\circ \text{ A}$$

$$I_{ca} = \frac{E_{CA}}{Z_{ca}} = I_{ab}(\angle 120^\circ) = 17.33\angle 96.87^\circ \text{ A}$$


Line Current:

$$I_{Aa} = I_{ab} - I_{ca} = I_{ab}(\sqrt{3}\angle -30^\circ)$$

$$= (17.33\angle -23.13^\circ)(\sqrt{3}\angle -30^\circ) = 30\angle -53.13^\circ \text{ A}$$

$$I_{Bb} = I_{bc} - I_{ab} = I_{bc}(\sqrt{3}\angle -30^\circ) = I_{Aa}(\angle -120^\circ) = 30\angle -173.13^\circ \text{ A}$$

$$I_{Cc} = I_{ca} - I_{bc} = I_{ca}(\sqrt{3}\angle -30^\circ) = I_{Aa}(\angle 120^\circ) = 30\angle 66.87^\circ \text{ A}$$

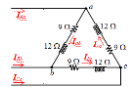**Power factor and Reactive factor:**

$$\theta = \theta_v - \theta_i = 30^\circ - (-23.13^\circ) = 53.13^\circ$$

$$pf = \cos \theta = \cos(53.13^\circ) = 0.6$$

$$rf = \sin \theta = \sin(53.13^\circ) = 0.8$$

Apparent Power, Real Power and Reactive Power

$$V_L = 260 \text{ V}; \quad I_L = 10 \text{ A}$$

$$S = \sqrt{3} V_L I_L = \sqrt{3} \times 260 \times 10 = 4503.3 \text{ VA}$$

$$P = \sqrt{3} V_L I_L \cos \theta = S \cos \theta = 4503.3 \times 0.6 = 2702 \text{ W}$$

$$Q = \sqrt{3} V_L I_L \sin \theta = S \sin \theta = 4503.3 \times 0.8 = 3602.7 \text{ VAR}$$


For same supply voltage and same per-phase impedance the power consumed by delta-connected load is 3 times higher than for wye-connected load. Thus we have

$$P_{\Delta} = 3P_Y$$

Converts Δ-connected load to Y-connected load:

$$Z_{ab} = Z_{bc} = Z_{ca} = Z_{\Delta} = 9 + j12 = 15\angle 53.13^\circ \Omega$$
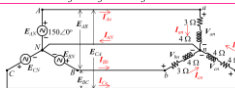
$$Z_u = Z_b = Z_c = Z_Y = \frac{Z_{\Delta}}{3} = \frac{9 + j12}{3} = 3 + j4 \Omega$$




Solve same as the Example (Y→Y)

Example (Δ→Δ)

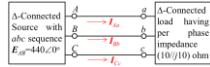Example ($\Delta \rightarrow \Delta$)

A three-phase Δ -connected balanced source with abc sequence is connected with a Δ -connected balanced load. In each phase, a $10\ \Omega$ resistance is connected in parallel with a capacitor having $10\ \Omega$ reactance. The phase voltage of source is given by $E_{ab}=440\angle 0^\circ\text{ V}$. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.



$$Z_{ab} = Z_{bc} = Z_{ca} = Z_Y = \frac{10 + (-j10)}{10 - j10} = 5 - j5 = 7.07\angle -45^\circ\ \Omega$$

For Δ connection: Phase Voltage = Line Voltage

$$E_{AB} = 440\angle 0^\circ\text{ V}$$

$$E_{BC} = E_{AB}(\angle -120^\circ) = 440\angle -120^\circ\text{ V}$$


$$E_{CA} = E_{AB}(\angle 120^\circ) = 440\angle 120^\circ\text{ V}$$

Phase Current:

$$I_{ab} = \frac{E_{AB}}{Z_{ab}} = \frac{440\angle 0^\circ}{7.07\angle -45^\circ} = 62.23\angle 45^\circ\text{ A}$$

$$I_{bc} = \frac{E_{BC}}{Z_{bc}} = I_{ab}(\angle -120^\circ) = 62.23\angle -75^\circ\text{ A}$$

$$I_{ca} = \frac{E_{CA}}{Z_{ca}} = I_{ab}(\angle 120^\circ) = 62.23\angle 165^\circ\text{ A}$$

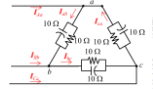**Line Current:**

$$I_{AB} = I_{ab} - I_{ca} = I_{ab}(\sqrt{3}\angle -30^\circ) = 108\angle 15^\circ\text{ A}$$

$$I_{BB} = I_{bc} - I_{ab} = I_{bc}(\sqrt{3}\angle -30^\circ) = I_{ab}(\angle -120^\circ) = 108\angle -105^\circ\text{ A}$$

$$I_{CA} = I_{ca} - I_{bc} = I_{ca}(\sqrt{3}\angle -30^\circ) = I_{ab}(\angle 120^\circ) = 108\angle 125^\circ\text{ A}$$

Power factor and Reactive factor:

$$\theta = \theta_v - \theta_i = 0^\circ - (-45^\circ) = -45^\circ$$

$$pf = \cos\theta = \cos(-45^\circ) = 0.707$$

$$rf = \sin\theta = \sin(-45^\circ) = -0.707$$

Apparent Power, Real Power and Reactive Power

$$V_L = 440\text{ V}; \quad I_L = 108\text{ A}$$


$$S = \sqrt{3}V_L I_L = \sqrt{3} \times 440 \times 108 = 82.3\text{ kVA}$$

$$P = \sqrt{3}V_L I_L \cos\theta = S \cos\theta = 82.3\text{ kVA} \times 0.707 = 58.2\text{ kW}$$

$$Q = \sqrt{3}V_L I_L \sin\theta = S \sin\theta = 82.3\text{ kVA} \times -0.707 = -58.2\text{ kVar}$$

Example ($\Delta \rightarrow Y$)**Example ($\Delta \rightarrow Y$)**

A three-phase Δ -connected balanced source with abc sequence is connected with a Y-connected balanced load having the per-phase impedance $5 + j5\ \Omega$. The phase voltage of source is given by $E_{ab}=440\angle 0^\circ\text{ V}$. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.

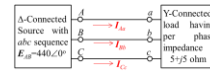**Power factor and Reactive factor:**

$$\theta = \theta_v - \theta_i = 0^\circ - (-45^\circ) = 45^\circ$$

$$pf = \cos\theta = \cos(45^\circ) = 0.707$$

$$rf = \sin\theta = \sin(45^\circ) = 0.707$$


Apparent Power, Real Power and Reactive Power

$$V_L = 440\text{ V}; \quad I_L = 36\text{ A}$$

$$S = \sqrt{3}V_L I_L = \sqrt{3} \times 440 \times 36 = 27.45\text{ kVA}$$

$$P = \sqrt{3}V_L I_L \cos\theta = S \cos\theta = 27.45\text{ kVA} \times 0.707 = 19.4\text{ kW}$$


$$Q = \sqrt{3}V_L I_L \sin\theta = S \sin\theta = 27.45\text{ kVA} \times 0.707 = 19.4\text{ kVar}$$

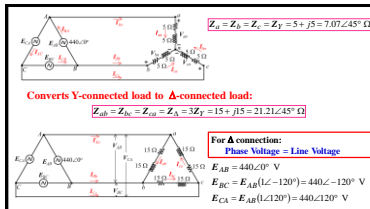**Phase Current:**

$$I_{ab} = \frac{E_{AB}}{Z_{ab}} = \frac{440\angle 0^\circ}{21.21\angle 45^\circ} = 20.74\angle -45^\circ\text{ A}$$

$$I_{bc} = \frac{E_{BC}}{Z_{bc}} = I_{ab}(\angle -120^\circ) = 20.74\angle -165^\circ\text{ A}$$

$$I_{ca} = \frac{E_{CA}}{Z_{ca}} = I_{ab}(\angle 120^\circ) = 20.74\angle 75^\circ\text{ A}$$

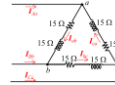**Line Current:**

$$I_{AB} = I_{ab} - I_{ca} = I_{ab}(\sqrt{3}\angle -30^\circ) = 36\angle -75^\circ\text{ A}$$

$$I_{BB} = I_{bc} - I_{ab} = I_{bc}(\sqrt{3}\angle -30^\circ) = I_{ab}(\angle -120^\circ) = 36\angle -195^\circ = 36\angle 165^\circ\text{ A}$$


$$I_{CA} = I_{ca} - I_{bc} = I_{ca}(\sqrt{3}\angle -30^\circ) = I_{ab}(\angle 120^\circ) = 36\angle 45^\circ\text{ A}$$

Converts Δ -connected source to Y-connected source:

$$E_{AB} = 440\angle 0^\circ \text{ V} \quad E_{BC} = E_{AB}(\angle -120^\circ) = 440\angle -120^\circ \text{ V}$$

$$E_{CA} = E_{AB}(\angle 120^\circ) = 440\angle 120^\circ \text{ V}$$

$$E_{AN} = E_{AB}\left(\frac{1}{\sqrt{3}}\angle -30^\circ\right) = 254\angle -30^\circ \quad E_{BN} = 254\angle -150^\circ \quad E_{CN} = 254\angle 90^\circ$$

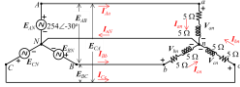Solve same as the Example (Y \rightarrow Y)**Example**

A 220 volts three-phase supply is connected with a Y-connected load having $R = 6 \Omega$ and $X_L = 8 \Omega$. (i) Find the line current, power per phase and total power. (ii) Find the phase voltages, phase currents and line voltages of the load in polar form considering abc sequence.

Solution

$$V_L = 220 \text{ V} \quad V_P = \frac{V_L}{\sqrt{3}} = \frac{220}{\sqrt{3}} = 127 \text{ V} \quad Z = Z_{am} = Z_{bm} = Z_{cn} = 6 + j8 = 10\angle 53.13^\circ \Omega$$

$$I_L = I_P = \frac{127}{10} = 12.7 \text{ A} \quad P = 3I_P^2 R = 3 \times 12.7^2 \times 6 = 3 \times 968 = 2904 \text{ W}$$

$$V_{am} = 127\angle 0^\circ \text{ V} \quad V_{bm} = 127\angle -120^\circ \text{ V} \quad V_{cn} = 127\angle 120^\circ \text{ V}$$

$$V_{ab} = 220\angle 30^\circ \text{ V} \quad V_{bc} = 220\angle -90^\circ \text{ V} \quad V_{ca} = 220\angle 150^\circ \text{ V}$$

$$I_{an} = I_{Ap} = \frac{V_{am}}{Z_p} = \frac{127\angle 0^\circ}{10\angle 53.13^\circ} = 12.7\angle -53.13^\circ \text{ A}$$

$$I_{bn} = I_{Bp} = 10\angle -173.13^\circ \text{ A} \quad I_{cn} = I_{Cp} = 10\angle 66.87^\circ \text{ A}$$

Example

A 220 volts three-phase supply is connected with a Δ -connected load having $R = 6 \Omega$ and $X_L = 8 \Omega$. (i) Find the line current, power per phase and total power. (ii) Find the phase voltages, phase currents and line voltages of the load in polar form considering abc sequence.

Solution

$$V_L = V_P = 220 \text{ V} \quad Z_{ab} = Z_{bc} = Z_{ca} = 6 + j8 = 10\angle 53.13^\circ \Omega \quad I_P = \frac{220}{10} = 22 \text{ A}$$

$$I_L = \sqrt{3} \times 22 = 38.1 \text{ A} \quad P = 3I_P^2 R = 3 \times 22^2 \times 6 = 8712 \text{ W}$$


$$V_{ab} = V_{ab} = 220\angle 0^\circ \text{ V} \quad V_{bc} = 220\angle -120^\circ \text{ V} \quad V_{ca} = 220\angle 120^\circ \text{ V}$$

$$I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{220\angle 0^\circ}{10\angle 53.13^\circ} = 22\angle -53.13^\circ \text{ A} \quad I_{bc} = 22\angle -173.13^\circ \text{ A} \quad I_{ca} = 22\angle 66.87^\circ \text{ A}$$

$$I_{An} = [\sqrt{3}\angle -30^\circ]I_{ab} = 38.1\angle -83.13^\circ \text{ A} \quad I_{Bn} = 38.1\angle -203.13^\circ \text{ A} \quad I_{Cn} = 38.1\angle 36.87^\circ \text{ A}$$

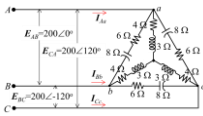Example

A balanced Y-connected load is connected in parallel with a balanced delta-connected load. The impedance of Y-load is $Z_Y = 4 + j3$ and the impedance of Δ -load is $Z_\Delta = 6 + j8$. Find the total average, reactive, and apparent power. In addition, find the power factor of the load.



$$\text{Solution: } Z_\Delta = 6 - j8 = 10\angle -53.13^\circ \Omega \quad Z_Y = 4 + j3 = 5\angle 36.87^\circ \Omega$$

$$Z_{Y-\Delta} = 3Z_Y = 12 + j9 = 15\angle 36.87^\circ \Omega$$

$$Z_{PA} = \frac{(10\angle -53.13^\circ)(5\angle 36.87^\circ)}{10\angle -53.13^\circ + 15\angle 36.87^\circ} = 8.3\angle -19.44^\circ = 7.85 - j2.77 \Omega$$

$$V_L = V_P = 200 \text{ V} \quad I_P = \frac{200}{8.3} = 24.1 \text{ A} \quad I_L = \sqrt{3} \times 24.1 = 42.74 \text{ A}$$

$$P = 3I_P^2 R = 3 \times 24.1^2 \times 7.85 = 13.68 \text{ kW}$$

$$Q = 3I_P^2 X = 3 \times 24.1^2 \times 2.77 = 4.84 \text{ kVar (Capacitive)}$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{(13.68)^2 + (4.84)^2} = 14.51 \text{ kVA}$$

$$\text{pf} = \frac{P}{S} = \frac{13.68}{14.51} = 0.94$$

Example

A three-phase motor takes 10 kVA to 0.6 power factor lagging from a source of 220 volts. It is in parallel with a balanced delta load having 16 ohms resistance and 12 ohms capacitive reactance in series in each phase. Find the total volt-amperes, power, line current and power factor of the combination.

$$\text{Solution: For Motor } S_m = 10 \text{ kVA} \quad \cos \theta_m = 0.6 \quad \sin \theta_m = \sqrt{1 - 0.6^2} = 0.8$$

$$P_m = S_m \cos \theta_m = 10 \times 0.6 = 6 \text{ kW} \quad Q_m = S_m \sin \theta_m = 10 \times 0.8 = 8 \text{ kVar}$$

$$I_{Lm} = \frac{S_m}{\sqrt{3}V_L} = \frac{10 \times 10^3}{\sqrt{3} \times 220} = 26.24 \text{ A}$$

$$\text{For Delta Load } Z_\Delta = \sqrt{16^2 + 12^2} = 20 \Omega \quad I_{PA} = \frac{220}{20} = 11 \text{ A} \quad I_{PA} = \sqrt{3} \times 11 = 19.1 \text{ A}$$

$$P_\Delta = 3 \times 11^2 \times 16 = 5.81 \text{ kW} \quad Q_\Delta = -3 \times 11^2 \times 12 = -4.36 \text{ kVar}$$

Total

$$P_T = P_m + P_\Delta = 6 + 5.81 = 11.81 \text{ kW}$$

$$Q_T = Q_m + Q_\Delta = 8 - 4.36 = 3.64 \text{ kVar}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \sqrt{(11.81)^2 + (3.64)^2} = 12.37 \text{ kVA}$$

$$\text{pf} = \frac{P_T}{S_T} = \frac{11.81}{12.37} = 0.955 \text{ (lagging)}$$

$$I_{LT} = \frac{S_T}{\sqrt{3}V_L} = \frac{12.37 \times 10^3}{\sqrt{3} \times 220} = 32.5 \text{ A}$$

Example

A three-phase motor takes 10 kVA to 0.6 power factor lagging from a source of 220 volts. Calculate the per phase impedance if the motor is connected (i) Y-connected, and (ii) Δ -connected.

$$\cos \theta = 0.6 \quad \sin \theta = \sqrt{1 - 0.6^2} = 0.8$$

$$\text{For Y-connection: } V_P = \frac{V_L}{\sqrt{3}} = \frac{220}{\sqrt{3}} = 127 \text{ V} \quad I_L = I_P = \frac{S}{\sqrt{3}V_L} = \frac{10 \times 10^3}{\sqrt{3} \times 220} = 26.24 \text{ A}$$

$$Z = \frac{V_P}{I_L} = \frac{127}{26.25} = 4.84 \Omega \quad R = Z \cos \theta = 4.84 \times 0.6 = 2.9 \Omega$$

$$X = Z \sin \theta = 4.84 \times 0.8 = 3.9 \Omega \quad Z = 2.9 + j3.9 \Omega$$

$$\text{For } \Delta\text{-connection: } V_P = V_L = 220 \text{ V} \quad I_L = \frac{S}{\sqrt{3}V_L} = \frac{10 \times 10^3}{\sqrt{3} \times 220} = 26.24 \text{ A}$$

$$I_P = \frac{I_L}{\sqrt{3}} = \frac{26.25}{\sqrt{3}} = 15.14 \text{ A} \quad Z = \frac{V_P}{I_P} = \frac{220}{15.14} = 14.52 \Omega$$

$$R = Z \cos \theta = 14.52 \times 0.6 = 8.7 \Omega \quad X = Z \sin \theta = 14.52 \times 0.8 = 11.6 \Omega \quad Z = 8.7 + j11.6 \Omega$$