

American International University-Bangladesh (AIUB)
Engineering Faculty
EEE 2101: Electrical Circuits-2 (AC)

Final Term Assignment 01 (Resonance Circuit) [Total 10 Marks]

Submission Date	Marks	Tick on following
With in April 26, 2017 [Exam day 5]	10	
April, 26, 2017 to May 2, 2017	5	
After May 2, 2017	0	

Polyphase Balanced System

- [Q1] How many ways the poly-phase system can be connected?
- [Q2] Show the star connection and mesh connection for a five phase source system.
- [Q3] With proper circuit diagram and vector diagram show the line voltage for a Y-connected *abc* sequence source is leads the phase voltage by 30° .
- [Q4] With proper circuit diagram and vector diagram show the line current for a Δ -connected *abc* sequence source is lags the phase current by 30° .
- [P1] If the line current is 120 A and line voltage is 440 V for a balanced five-phase system, find the magnitude of the phase voltage and the phase current for (i) the star-connection, and (ii) the mesh-connection.
- [P2] A three-phase Y-connected balanced source with *abc* sequence is connected with a Y-connected balanced load having the per phase impedance $10+j20 \Omega$. The neutrals of both source and load are connected. The phase voltage of source is given by $E_{an}=250\angle 0^\circ$ V. Calculate (i) the phase voltages (V_{an}, V_{bn}, V_{cn}), (ii) the line voltages (E_{AB}, E_{BC}, E_{CA}), (iii) the phase currents (I_{an}, I_{bn}, I_{cn}), (iv) the line currents (I_{Aa}, I_{Bb}, I_{Cc}), (v) the power factor and reactive factor, (vi) the power, reactive power and apparent power, and (vii) Draw the vector diagram by showing all phase and line voltages and phase current and line currents.
- [P3] A three-phase Δ -connected balanced source with *abc* sequence is connected with a Δ -connected balanced load. In each phase, a 20 ohm resistance is connected in parallel with a capacitor having 15 ohm reactance. The phase voltage of source is given by $E_{AB}=220\angle 0^\circ$ V. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, (vi) the power, reactive power and apparent power, and (vii) Draw the vector diagram by showing all phase and line voltages and phase current and line currents.
- [P4] A three-phase Y-connected balanced source with *abc* sequence is connected with a Δ -connected balanced load having the per phase impedance $12-j9 \Omega$. The phase voltage of source is given by $E_{an}=200\angle 0^\circ$ V. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.

[P5] A three-phase Δ -connected balanced source with abc sequence is connected with a Y-connected balanced load having the per-phase impedance $3+j4$ ohm. The phase voltage of source is given by $E_{AB}=110\angle 0^\circ$ V. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.

[P6] A three-phase motor takes 10 kW to 0.7 power factor lagging from a source of 440 volts. It is in parallel with a balanced delta load having 18 ohms resistance and 24 ohms inductive reactance in series in each phase. Find the total volt-amperes, power, line current and power factor of the combination.

Power Measurement of Polyphase System

[Q1] With vector diagram by using the two wattmeter method the measured power is given by: $(\sqrt{3})V_L I_L \cos \theta$.

[Q2] Write the mathematical expression of (i) real power, (ii) reactive power, (iii) power factor angle, and (iv) power factor in terms of the two watt meters reading of W_a and W_b .

[Q4] Draw the power factor vs watt-ratio curve.

[Q5] Explain the significance of (i) equal wattmeter readings, (ii) a zero reading on one wattmeter, (iii) reading of W_a is greater than the reading of W_b , and (iv) reading of W_b is greater than the reading of W_a .


[P1] The two wattmeter method produces wattmeter readings are 1560 W and 2100 W when connected to balanced delta-connected load. If the line voltage is 220 V, calculate (i) the per-phase power, (ii) the per-phase reactive power, (iii) the power factor, and (iv) the phase impedance.

[P2] Let the line voltage 208 V and the wattmeter readings of the balanced system are -560 W and 800 W. Determine (i) the total power, (ii) the total reactive power, (iii) the power factor, (iv) the phase impedance, and (v) Is the impedance inductive or capacitive.


[P3] In a three phase circuit, the wattmeter W_a reads 300 watts and W_b reads 500 watts. When the potential coil of W_c is disconnected at c and connected at b , the needle goes against the down-scale stop. Calculate the total power, watt ratio, reactive power, apparent power and power factor.

[P4] A three-phase, 250 V motor load has a power factor of 0.8. Two wattmeters connected to measure the power show the input to be 40 kW. Find the reading on each instrument.

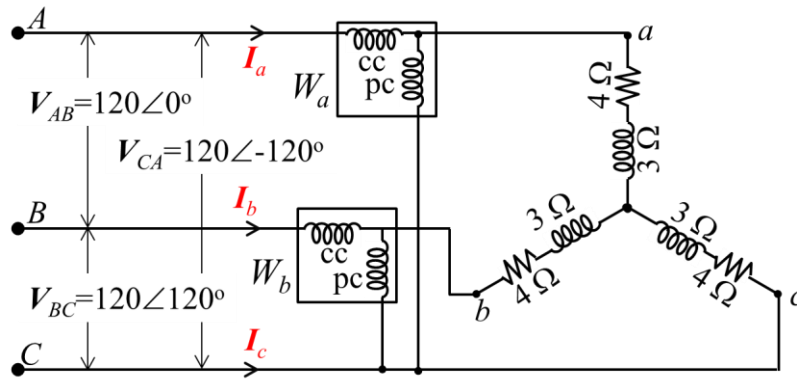[P5] For the balanced Y-connected load of following figures with two properly connected wattmeters: (i) Determine the power reading of each wattmeter. (iv) Calculate the total power absorbed by the load. (v) Compare the result of part (iv) with the total power calculated using the phase currents and the resistive elements.




[P6] For the unbalanced delta-connected load of following figures with two properly connected wattmeters: (i) Determine the magnitude and angle of the phase currents. (ii) Calculate the magnitude and angle of the line currents. (iii) Determine the power reading of each wattmeter. (iv) Calculate the total power absorbed by the load. (v) Compare the result of part (iv) with the total power calculated using the phase currents and the resistive elements.

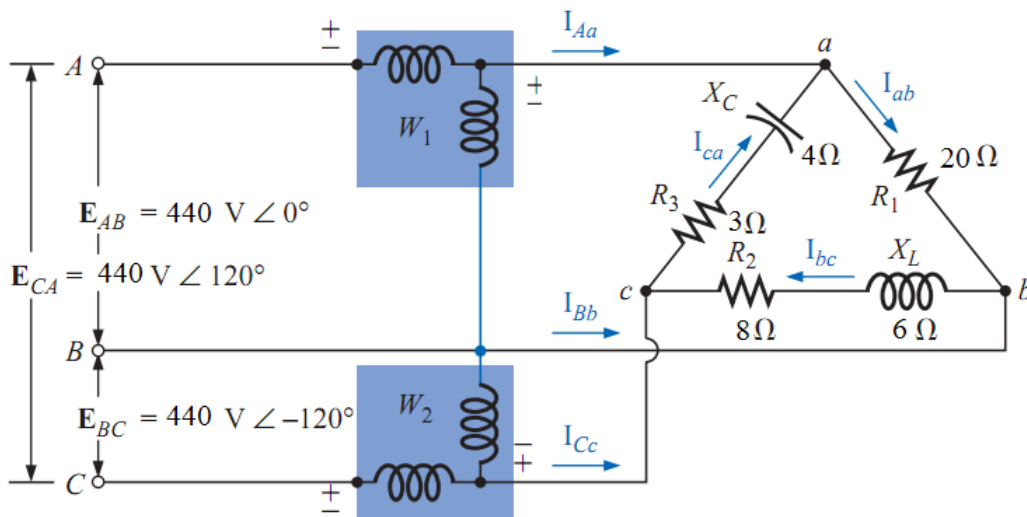


Polyphase Unbalanced System

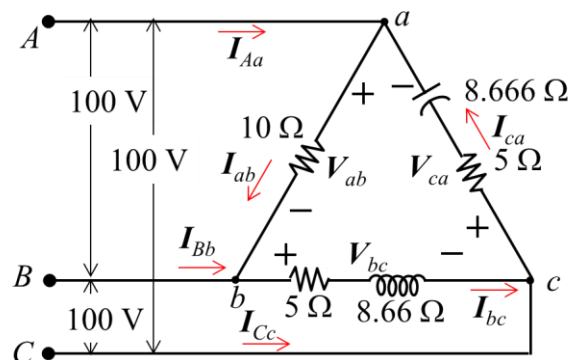
[P1] A balanced three-phase source of 100 V is connected with an unbalanced Δ -connected load as shown in the following figure. Calculate (i) the phase currents (I_{ab} , I_{bc} , I_{ca}), (ii) the line currents (I_{Aa} , I_{Bb} , I_{Cc}), (iii) the overall power, reactive power, apparent power.



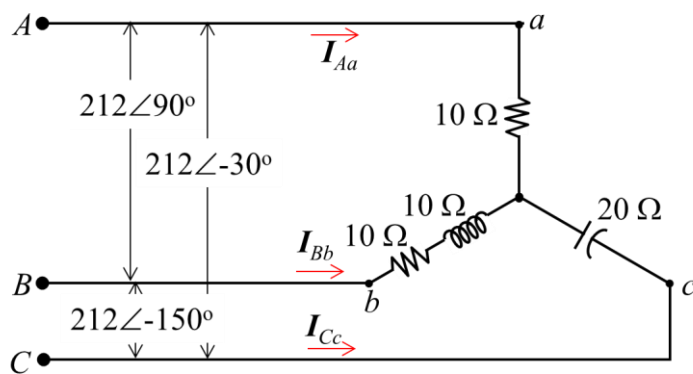[P2] A balanced three-phase source of 212 V is connected with an unbalanced Y-connected load as shown in the following figure. Calculate (i) the line currents (I_{Aa} , I_{Bb} , I_{Cc}), and (ii) the overall power, reactive power, apparent power.



[P3] Refer to the following figure, E_{AN} , E_{BN} , and E_{CN} are balanced three-phase voltages with magnitude of 115.4 volts and a phase sequence the sequence of ABC. Calculate (i) the phase voltages of load (V_{ab} , V_{bc} , V_{ca}), (ii) the phase currents of load (I_{ab} , I_{bc} , I_{ca}), (iii) the line currents (I_{Aa} , I_{Bb} , I_{Cc}). (iv) the total power, reactive power, and apparent power.

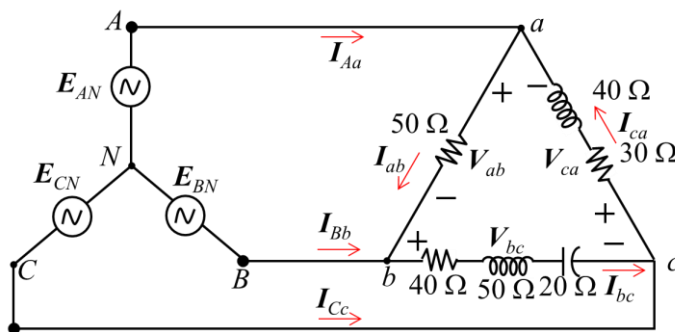

Coupling Circuit

[Q1] Define coupling circuit. Classify the coupling circuit.

[Q2] Define magnetic coupling circuit, self-flux, leakage flux and mutual flux.

[Q3] Explain briefly explain how to identify the sign of mutual inductance.


[Q4] Define coupling co-efficient. Based on the range of coupling coefficient of a magnetic circuit define the perfectly coupling, tightly coupling and loosely coupling circuits.

[Q5] Define transformer, primary side and secondary side.


[P1] Two similar coils have a coupling coefficient of 0.25. When they are connected cumulatively in series, the total inductance is 80 mH. Calculate the self-inductance inductance of each coil. Also, calculate the total inductance when the coils are differentially connected in series.

[P2] Two inductively coupled coils have self-inductances 7.5 H and 25 H. If the coupling coefficient is 0.8 (i) find the value of mutual inductance between the coils, and (ii) what is the maximum possible mutual inductance?

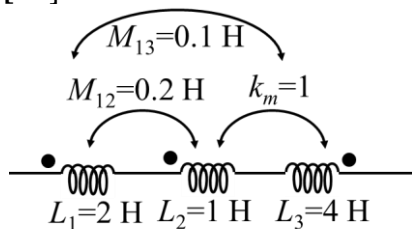
[P3] Find the total inductance of the series coils of following Figures.



(a)

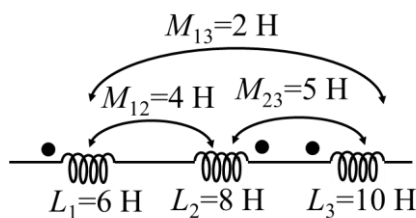


(b)

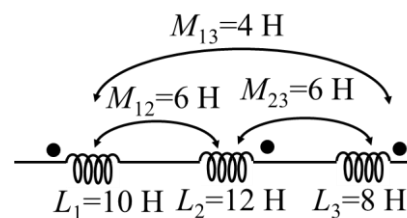


(c)

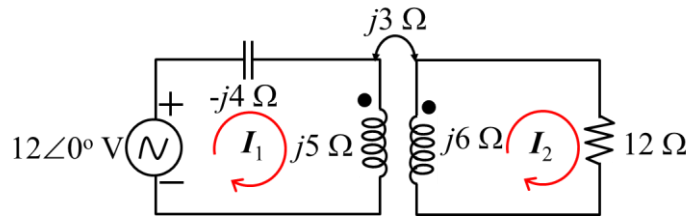[P4] For the following circuits write the loop equations and calculate (i) the currents, I_1 , and I_2 , and (ii) the equivalent impedance. and (iii) the consumed power.



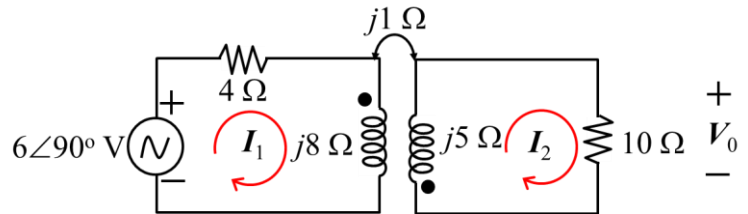[P5] For the following circuits write the loop equations and calculate (i) the currents, I_1 , I_2 , and V_0 , and (ii) the equivalent impedance. and (iii) the consumed power.



[P6] For the following circuits write the loop equations and calculate (i) the currents, I_1 , and I_2 , and (ii) the equivalent impedance. and (iii) the consumed power.

