

Parallel Circuits

Prepared by

Dr. Mohammad Abdul Mannan

Professor, Department of EEE

American International University – Bangladesh (AIUB)

Admittance

The reciprocal of **impedance** is called **admittance**.

The unit of admittance is **Siemens** [S].

$$Y = \frac{1}{Z} = \frac{I}{V} = Y \angle \theta_y = G + jB = g + jb = (\text{Conducacne}) + j(\text{Susceptance}) \text{ [S]}$$

$$\text{Conducacne : } G = g = Y \cos \theta_y \text{ [S]} \quad \text{Susceptance : } B = b = Y \sin \theta_y \text{ [S]}$$

G or g is called conductance. The unit of conductance is **mho** or **Siemens**.
Conductance (*G* or *g*) is the reciprocal of resistance (*R*).

B or b is called susceptance. The unit of susceptance is **Siemens**.
Susceptance (*B* or *b*) is the reciprocal of reactance (*X*).

$$G = g = \frac{1}{R} \text{ [S]} \quad B = b = \frac{1}{X} \text{ [S]} \quad B_L = b_L = \frac{1}{X_L} \text{ [S]} \quad B_C = b_C = \frac{1}{X_C} \text{ [S]}$$

B_L or b_L is called inductive susceptance.

B_C or b_C is called capacitive susceptance.

Admittance of a Resistance, Inductance and Capacitance

Admittance of a resistance:

$$Y_R = \frac{1}{Z_R} = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ \text{ [S]}$$

Admittance of an inductance:

$$Y_L = \frac{1}{Z_L} = \frac{1}{X_L \angle 90^\circ} = B_L \angle -90^\circ \text{ [S]}$$

Admittance of a capacitance:

$$Y_C = \frac{1}{Z_C} = \frac{1}{X_C \angle -90^\circ} = B_C \angle 90^\circ \text{ [S]}$$

Admittance of a RL series branch:

$$Y_{RL} = \frac{1}{Z_{RL}} = \frac{1}{R \angle 0^\circ + X_L \angle 90^\circ} = \frac{1}{R + jX_L} \text{ [S]}$$

Admittance of a RC series branch:


$$Y_{RC} = \frac{1}{Z_{RC}} = \frac{1}{R \angle 0^\circ + X_C \angle -90^\circ} = \frac{1}{R - jX_C} \text{ [S]}$$

Admittance of a RLC series branch:

$$Y_{RLC} = \frac{1}{Z_{RLC}} = \frac{1}{R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ} = \frac{1}{R + jX_L - jX_C} \text{ [S]}$$

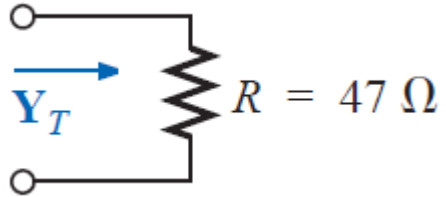
Example

Calculate the total admittance for the following circuit.




$$Z_T = 47 \angle 0^\circ \, \Omega$$
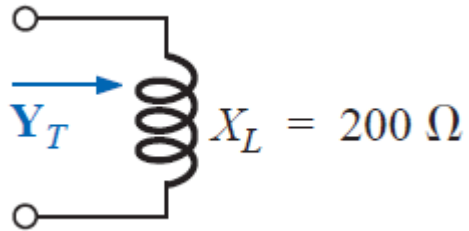
$$Y_T = \frac{1}{47 \angle 0^\circ} = 0.0213 \angle 0^\circ \, [S]$$



$$Z_T = 200 \angle 90^\circ \, \Omega$$
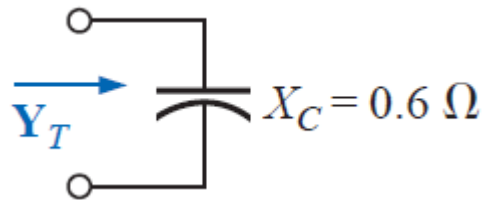
$$Y_T = \frac{1}{200 \angle 90^\circ} = 0.005 \angle -90^\circ \, [S]$$




$$Z_T = 0.6 \angle -90^\circ \, \Omega$$

$$Y_T = \frac{1}{0.6 \angle -90^\circ} = 1.67 \angle 90^\circ \, [S]$$

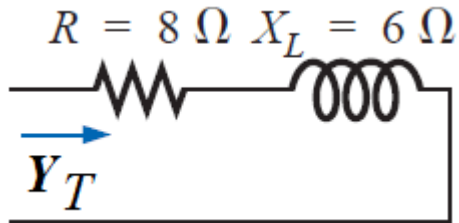
Example

Calculate the total admittance for the following circuit.




$$Z_T = 8 + j6 \Omega$$
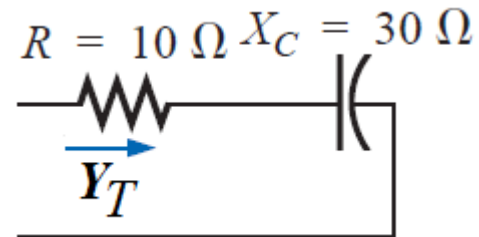
$$Y_T = \frac{1}{8 + j6} = 0.08 - j0.06 \text{ [S]}$$



$$Z_T = 10 - j30 \Omega$$
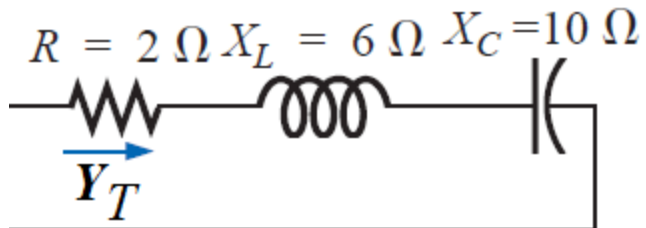
$$Y_T = \frac{1}{10 - j30} = 0.01 + j0.03 \text{ [S]}$$









$$Z_T = 2 + j6 - j10 \Omega$$

$$Y_T = \frac{1}{2 + j6 - j10} = \frac{1}{2 - j4} = 0.1 + j0.2 \text{ [S]}$$

Home Work 5.1

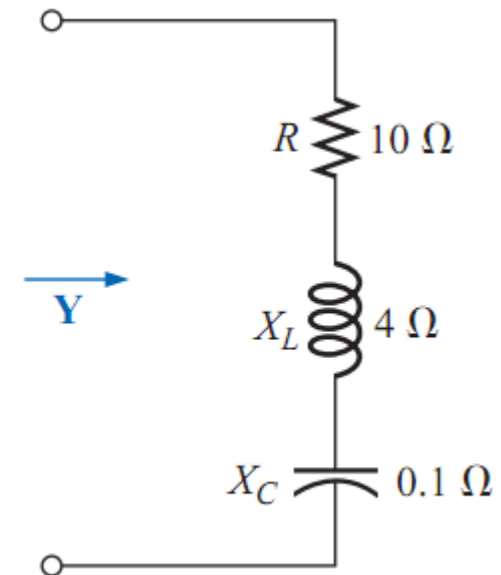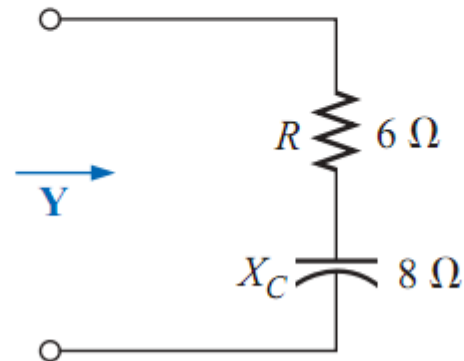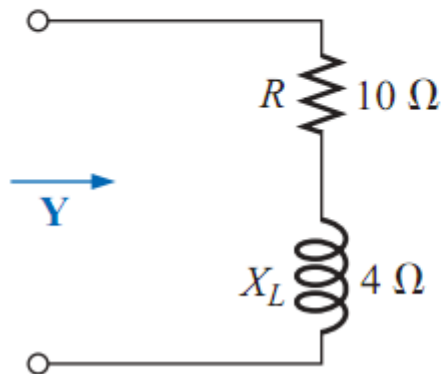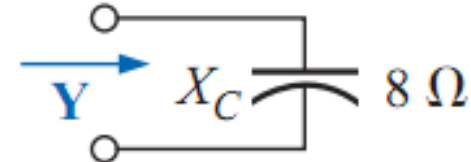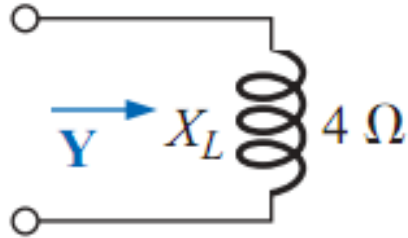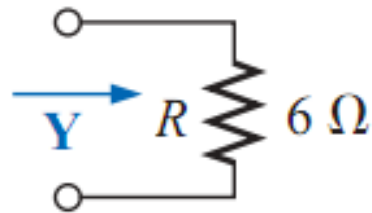Problem 1: Calculate the total admittance for the following circuit.




Admittance and Impedance of a *RL* Parallel Circuit

Admittance of a *RL* parallel Circuit:

$$Y = Y_{RL} = Y_R + Y_L = \frac{1}{R \angle 0^\circ} + \frac{1}{X_L \angle 90^\circ} \quad [S]$$
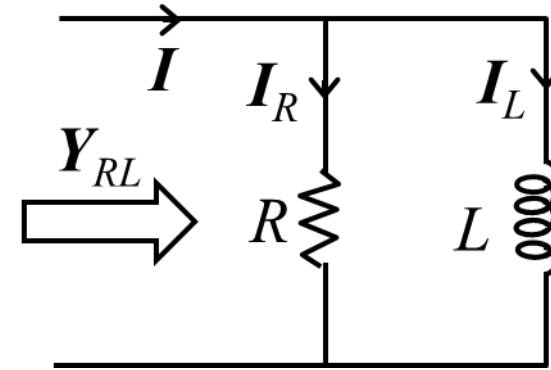
$$Y = Y_{RL} = G \angle 0^\circ + B_L \angle -90^\circ = G - jB_L \quad [S]$$



Impedance of a *RL* Parallel Circuit:

$$Z_{RL} = \frac{1}{Y_{RL}} = \frac{1}{Y_R + Y_L} = \frac{1}{\frac{1}{R \angle 0^\circ} + \frac{1}{X_L \angle 90^\circ}} = \frac{1}{\frac{1}{R} + \frac{1}{jX_L}} = \frac{(R)(jX_L)}{R + jX_L} \quad [\Omega]$$

$$Z_{RL} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L}} = \frac{Z_R Z_L}{Z_R + Z_L} \quad [\Omega]$$

Example



Calculate the total admittance and current for the following circuit.

$$G = \frac{1}{3.33} = 0.3 \text{ [S]} \quad B_L = \frac{1}{2.5} = 0.4 \text{ [S]}$$

$$Y_R = 0.3 \angle 0^\circ = 0.3 \text{ [S]} \quad Y_L = 0.4 \angle -90^\circ = -j0.4 \text{ [S]}$$

$$Y = 0.3 \angle 0^\circ + 0.4 \angle -90^\circ = 0.3 - j0.4 = 0.5 \angle -53.13^\circ \text{ [S]}$$
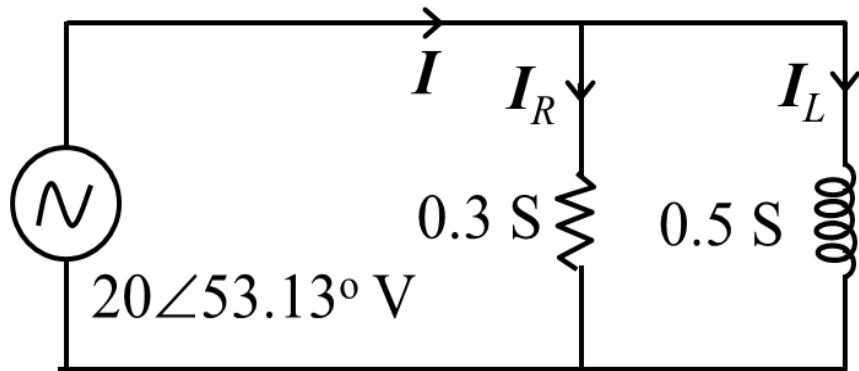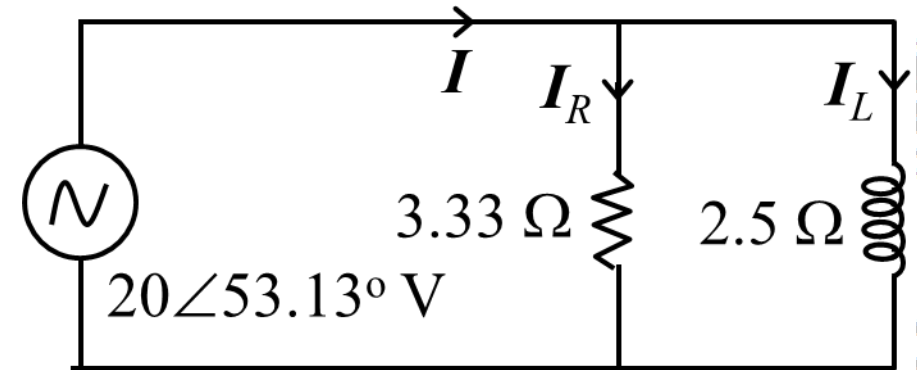
$$Z = \frac{1}{Y} = \frac{1}{0.5 \angle -53.13^\circ} = 2 \angle 53.13^\circ \text{ [\Omega]}$$



$$I = \frac{V}{Z} = YV = (0.5 \angle -53.13^\circ)(20 \angle 53.13^\circ) = 10 \angle 0^\circ \text{ [A]}$$

$$I_R = \frac{V}{Z_R} = Y_R V = (0.3 \angle 0^\circ)(20 \angle 53.13^\circ) = 6 \angle 53.13^\circ \text{ [A]}$$

$$I_L = \frac{V}{Z_L} = Y_L V = (0.4 \angle -90^\circ)(20 \angle 53.13^\circ) = 8 \angle -36.87^\circ \text{ [A]}$$

$$\theta = \theta_v - \theta_i = 53.13^\circ - 0^\circ = 53.13^\circ$$

$$pf = \cos(53.13^\circ) = 0.6 \text{ lagging}$$


$$rf = \sin(53.13^\circ) = 0.8$$

$$S = VI = 20 \times 10 = 200 \text{ VA}$$


$$P = VI \cos \theta = 20 \times 10 \times 0.6 = 120 \text{ W}$$

$$Q = VI \sin \theta = 20 \times 10 \times 0.8 = 160 \text{ VAR}$$

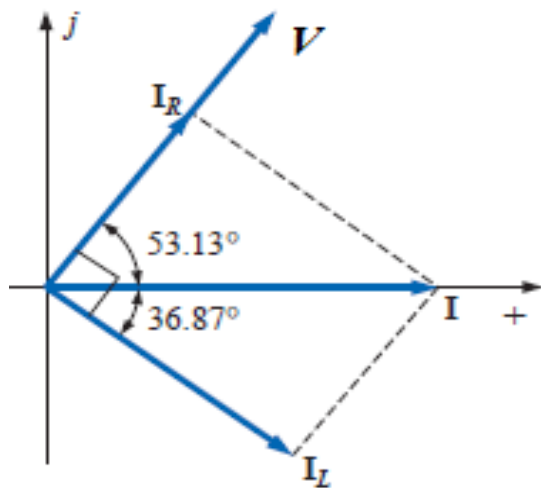
$$p(t) = 120(1 - \cos 2\omega t) + 160 \sin 2\omega t$$



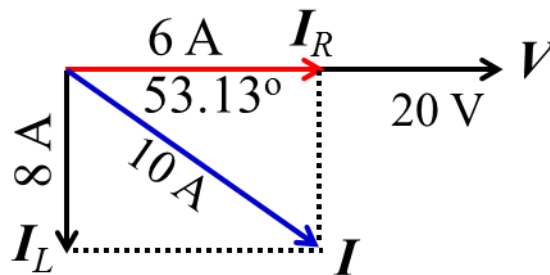
$$Q = I_L^2 X_L = 8^2 \times 2.5 = 160 \text{ VAR}$$



Phasor Diagram

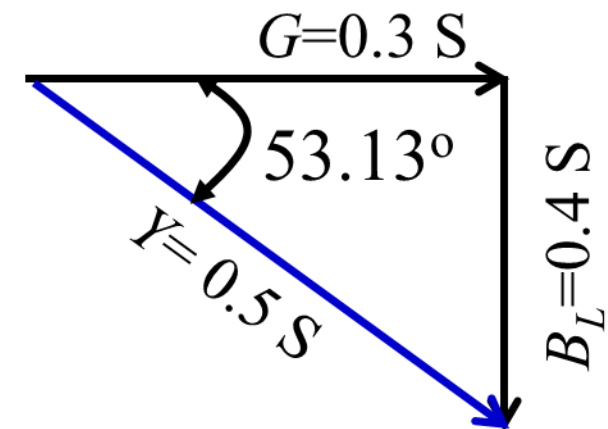

Admittance Diagram

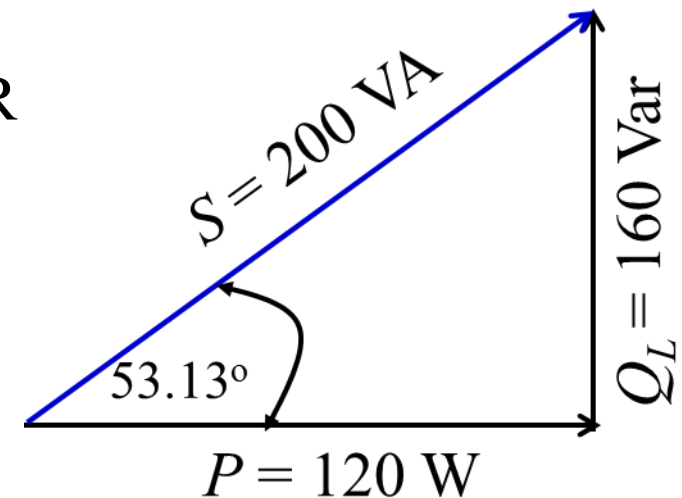


Power Triangle

Admittance and Impedance of a *RC* Parallel Circuit

Admittance of a *RC* parallel Circuit:

$$Y = Y_{RC} = Y_C + Y_R = \frac{1}{R \angle 0^\circ} + \frac{1}{X_C \angle -90^\circ} \quad [S]$$
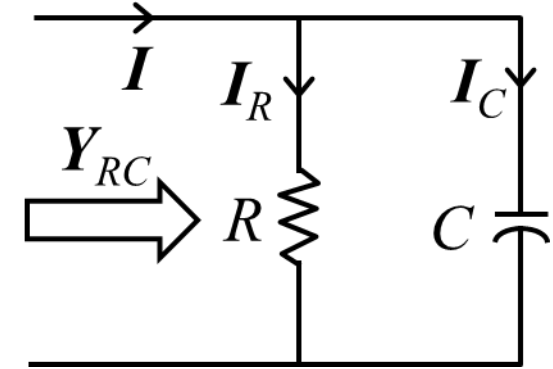
$$Y = Y_{RC} = G \angle 0^\circ + B_C \angle 90^\circ = G + jB_C \quad [S]$$



Impedance of a *RC* Parallel Circuit:

$$Z_{RC} = \frac{1}{Y_{RC}} = \frac{1}{Y_R + Y_C} = \frac{1}{\frac{1}{R \angle 0^\circ} + \frac{1}{X_C \angle -90^\circ}} = \frac{1}{\frac{1}{R} + \frac{1}{-jX_C}} = \frac{(R)(-jX_C)}{R - jX_C} \quad [\Omega]$$

$$Z_{RC} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_C}} = \frac{Z_R Z_C}{Z_R + Z_C} \quad [\Omega]$$

Example



Calculate the total admittance and current for the following circuit.

$$G = \frac{1}{1.67} = 0.6 \text{ [S]} \quad B_C = \frac{1}{1.25} = 0.8 \text{ [S]}$$

$$Y_R = 0.6 \angle 0^\circ = 0.6 \text{ [S]} \quad Y_C = 0.8 \angle 90^\circ = j0.8 \text{ [S]}$$

$$Y = 0.6 \angle 0^\circ + 0.8 \angle 90^\circ = 0.6 + j0.8 = 1.0 \angle 53.13^\circ \text{ [S]}$$
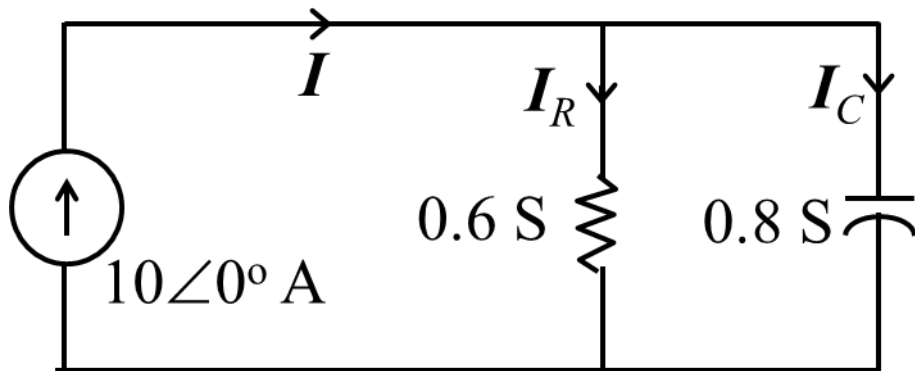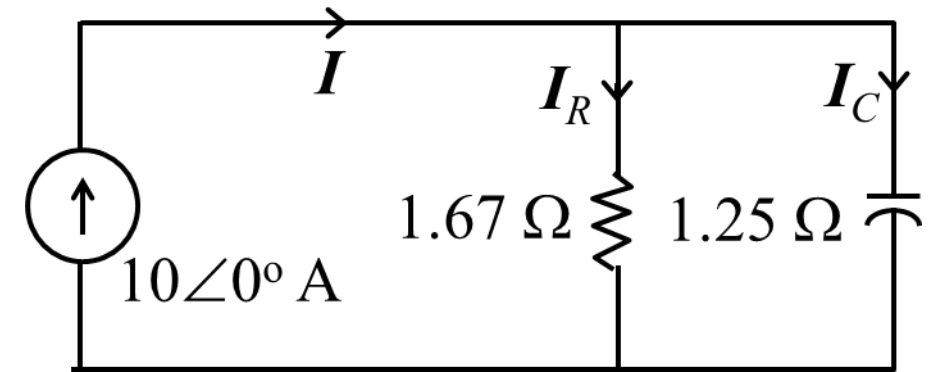
$$Z = \frac{1}{Y} = \frac{1}{1 \angle 53.13^\circ} = 1 \angle -53.13^\circ \text{ [\Omega]}$$



$$V = IZ = \frac{I}{Y} = \frac{10 \angle 0^\circ}{1 \angle 53.13^\circ} = 10 \angle -53.13^\circ \text{ [V]}$$

$$I_R = Y_R V = (0.6 \angle 0^\circ)(10 \angle -53.13^\circ) = 6 \angle -53.13^\circ \text{ [A]}$$

$$I_C = Y_C V = (0.8 \angle 90^\circ)(10 \angle -53.13^\circ) = 8 \angle 36.87^\circ \text{ [A]}$$

$$\theta = \theta_v - \theta_i = -53.13^\circ - 0^\circ = -53.13^\circ$$

$$pf = \cos(-53.13^\circ) = 0.6 \text{ leading}$$

$$rf = \sin(-53.13^\circ) = -0.8$$


$$S = VI = 10 \times 10 = 100 \text{ VA}$$

$$P = VI \cos \theta = 10 \times 10 \times 0.6 = 60 \text{ W}$$



$$Q = VI \sin \theta = 10 \times 10 \times -0.8 = -80 \text{ VAR}$$

$$p(t) = 60(1 - \cos 2\omega t) - 80 \sin 2\omega t$$

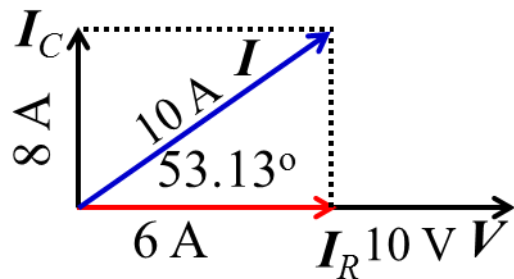
$$Q = I_C^2 X_C = 8^2 \times 1.25 = 80 \text{ VAR}$$



Phasor Diagram

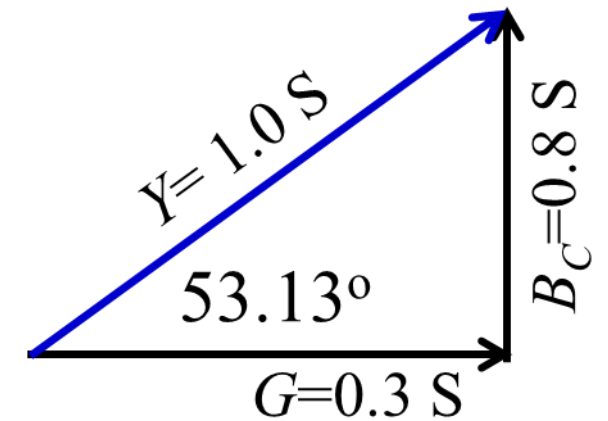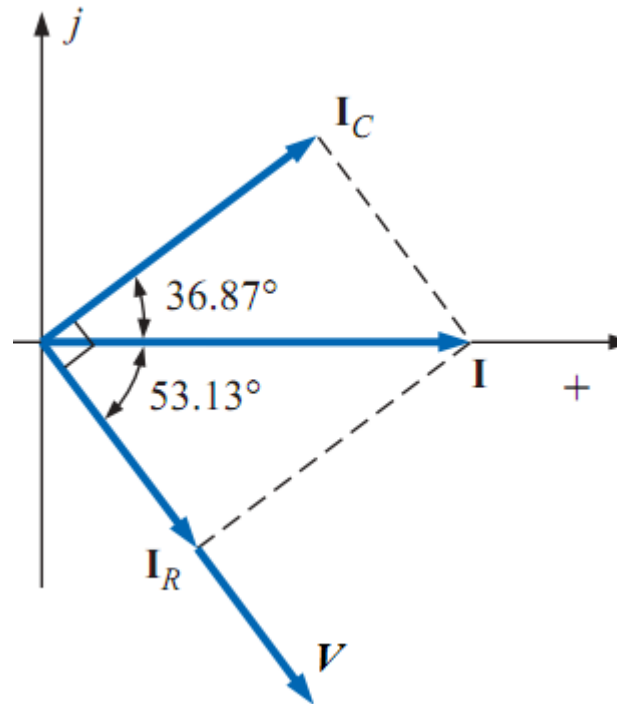

Admittance Diagram

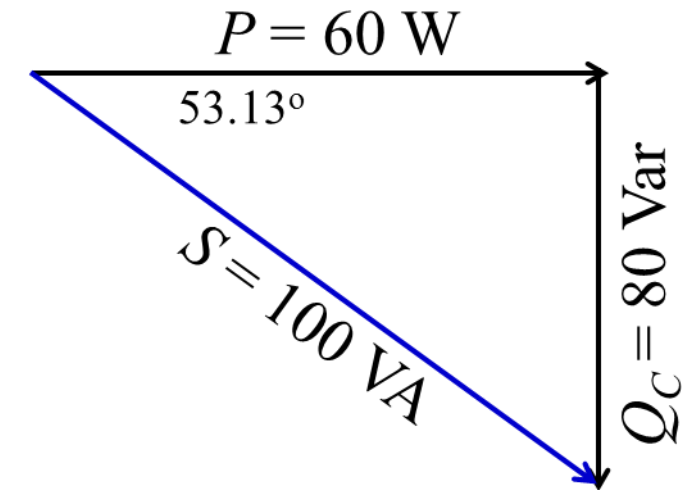


Power Triangle

Admittance and Impedance of a *RLC* Parallel Circuit

Admittance of a *RLC* parallel Circuit:
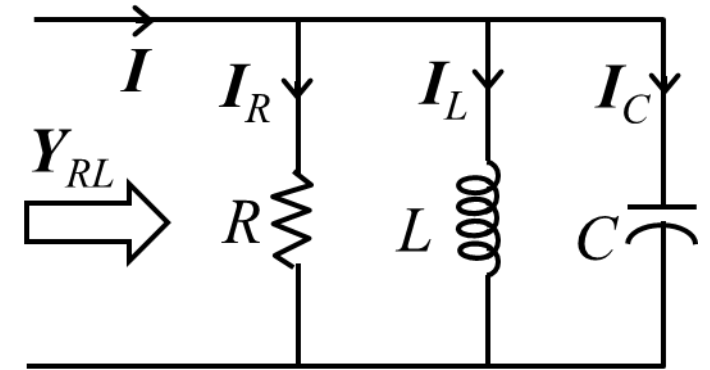
$$\begin{aligned} Y &= Y_{RLC} = Y_R + Y_L + Y_C \\ &= \frac{1}{R \angle 0^\circ} + \frac{1}{X_L \angle 90^\circ} + \frac{1}{X_C \angle -90^\circ} \quad [S] \end{aligned}$$



$$Y = Y_{RLC} = G \angle 0^\circ + B_L \angle -90^\circ + B_C \angle 90^\circ = G - jB_L + jB_C \quad [S]$$

Impedance of a *RLC* Parallel Circuit:

$$\begin{aligned} Z_{RLC} &= \frac{1}{Y_{RLC}} = \frac{1}{Y_R + Y_L + Y_C} \\ &= \frac{1}{\frac{1}{R \angle 0^\circ} + \frac{1}{X_L \angle 90^\circ} + \frac{1}{X_C \angle -90^\circ}} = \frac{1}{\frac{1}{R} + \frac{1}{jX_L} + \frac{1}{-jX_C}} \end{aligned}$$

$$Z_{RLC} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}}$$

Example

Calculate the total admittance and current for the following circuit.

$$G = \frac{1}{3.33} = 0.3 \text{ [S]} \quad B_L = \frac{1}{1.43} = 0.7 \text{ [S]}$$


$$B_C = \frac{1}{3.33} = 0.3 \text{ [S]}$$

$$Y_R = 0.3 \angle 0^\circ = 0.3 \text{ [S]}$$


$$Y_L = 0.7 \angle -90^\circ = -j0.7 \text{ [S]}$$

$$Y_C = 0.3 \angle 90^\circ = j0.3 \text{ [S]}$$
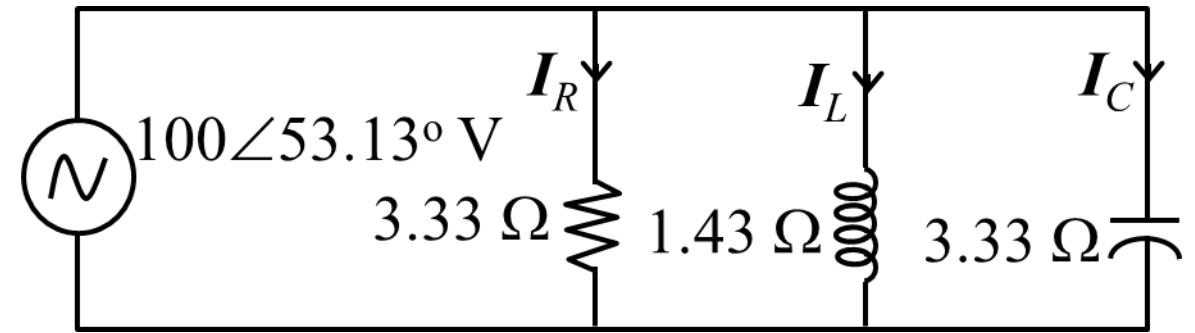
$$Z = \frac{1}{Y} = \frac{1}{0.5 \angle -53.13^\circ} = 2 \angle 53.13^\circ \text{ [\Omega]}$$


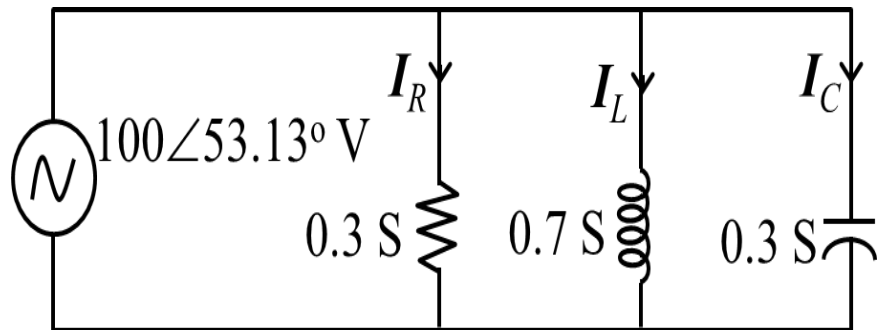
$$\begin{aligned} Y &= 0.3 \angle 0^\circ + 0.7 \angle -90^\circ + 0.3 \angle 90^\circ \\ &= 0.3 - j0.4 = 0.5 \angle -53.13^\circ \text{ [S]} \end{aligned}$$



$$I = VY = (100 \angle 53.13^\circ)(0.5 \angle -53.13^\circ) = 50 \angle 0^\circ \text{ [A]}$$

$$I_R = Y_R V = (0.3 \angle 0^\circ)(100 \angle 53.13^\circ) = 30 \angle 53.13^\circ \text{ [A]}$$

$$I_L = Y_L V = (0.7 \angle -90^\circ)(100 \angle 53.13^\circ) = 70 \angle -36.87^\circ \text{ [A]}$$

$$I_C = Y_C V = (0.3 \angle 90^\circ)(100 \angle 53.13^\circ) = 30 \angle 143.13^\circ \text{ [A]}$$

$$\theta = \theta_v - \theta_i = 53.13^\circ - 0^\circ = 53.13^\circ$$


$$pf = \cos(53.13^\circ) = 0.6 \text{ leading}$$

$$rf = \sin(53.13^\circ) = 0.8$$

$$S = VI = 100 \times 50 = 5000 \text{ VA}$$

$$P = VI \cos \theta = 100 \times 50 \times 0.6 = 3000 \text{ W}$$
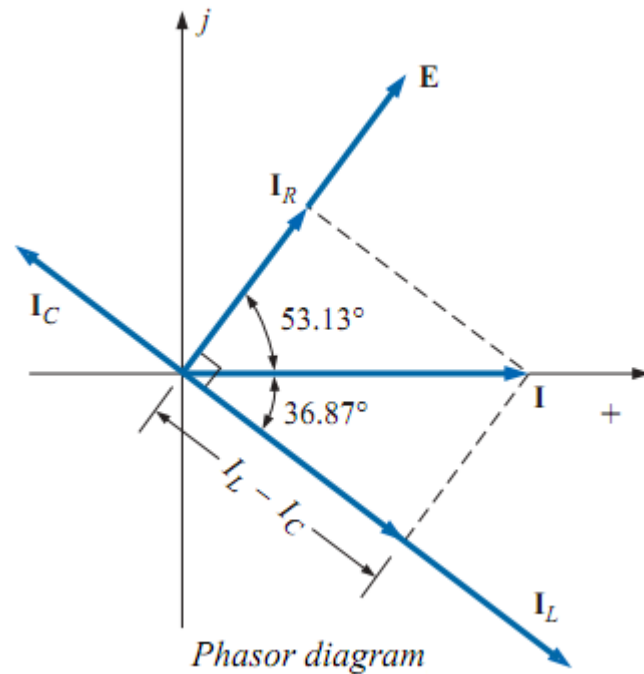
$$Q = VI \sin \theta = 100 \times 50 \times 0.8 = 4000 \text{ VAR}$$




$$p(t) = 3000(1 - \cos 2\omega t) + 4000 \sin 2\omega t$$

$$Q_L = I_L^2 X_L = 70^2 \times 1.43 = 7007 \text{ VAR}$$

$$Q_C = I_C^2 X_C = 30^2 \times 3.33 = 2997 \text{ VAR}$$
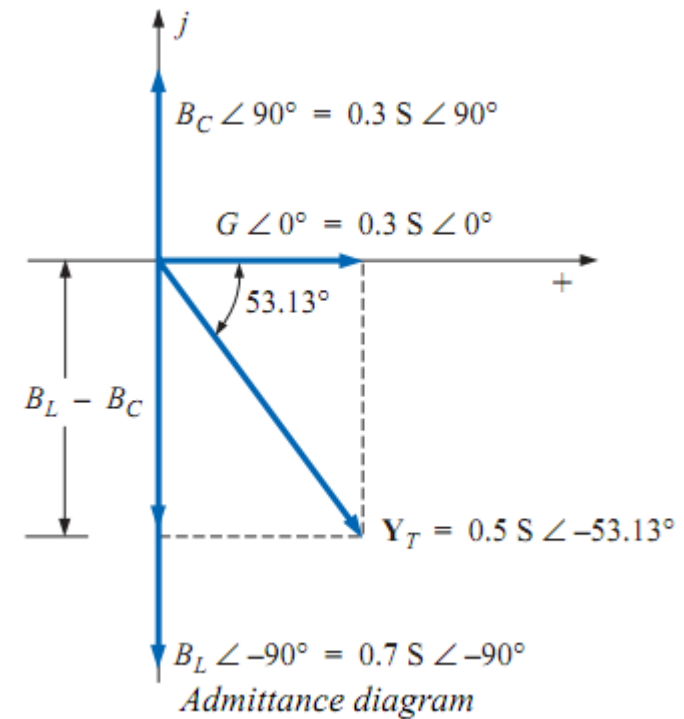
$$Q = Q_C - Q_C = 7007 - 2997 = 4010 \text{ VAR}$$



$$I = 50\angle 0^\circ \text{ [A]}$$

$$I_R = 30\angle 53.13^\circ \text{ [A]}$$

$$I_L = 70\angle -36.87^\circ \text{ [A]}$$


$$I_C = 30\angle 143.13^\circ \text{ [A]}$$

$$i(t) = \sqrt{2}(50)\sin \omega t = 70.7 \sin \omega t \text{ [A]}$$

$$i_R(t) = \sqrt{2}(30)\sin(\omega t + 53.13^\circ) = 42.42 \sin(\omega t + 53.13^\circ) \text{ [A]}$$

$$i_L(t) = \sqrt{2}(70)\sin(\omega t - 36.87^\circ) = 98.98 \sin(\omega t - 36.87^\circ) \text{ [A]}$$
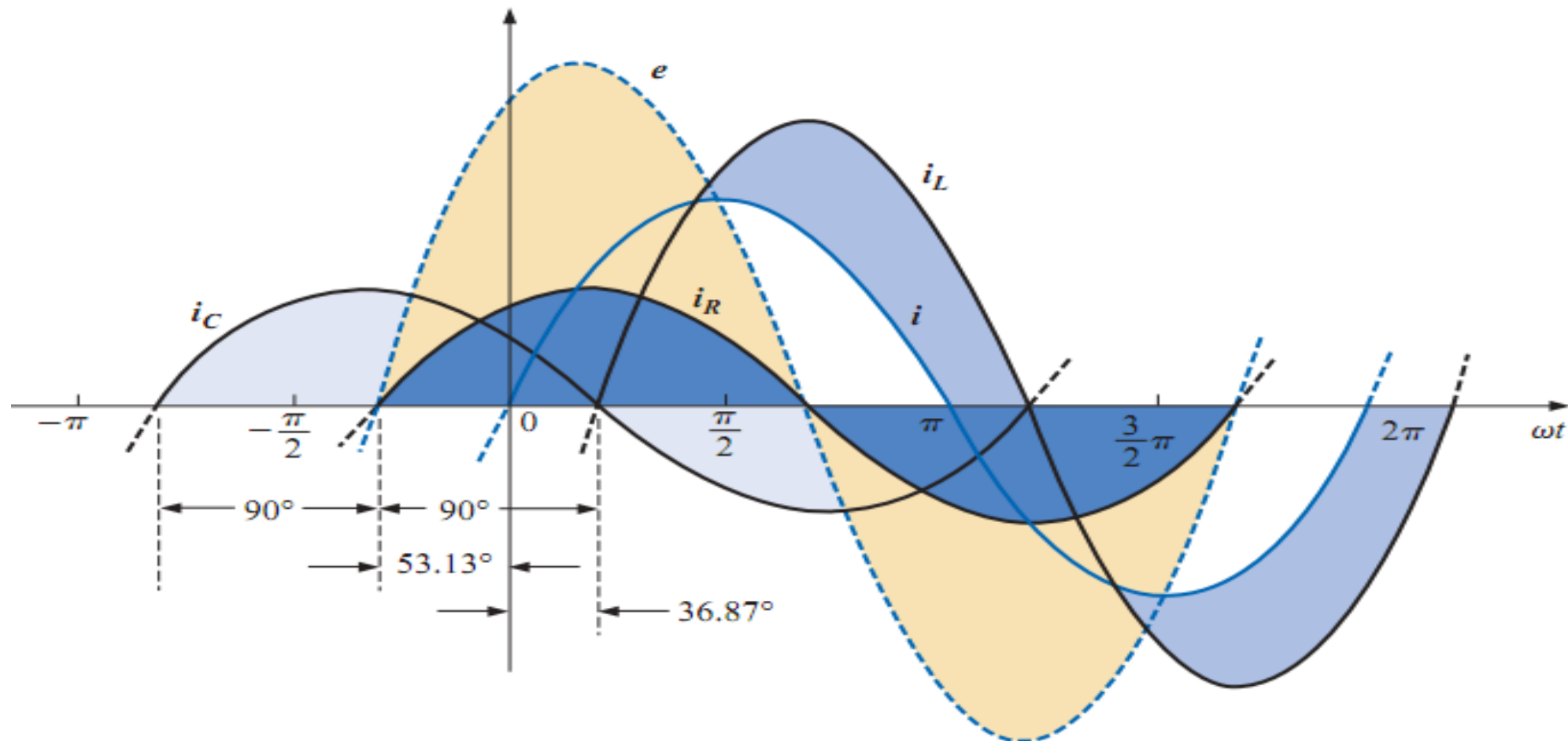
$$i_C(t) = \sqrt{2}(30)\sin(\omega t + 143.13^\circ) = 42.42 \sin(\omega t + 143.13^\circ) \text{ [A]}$$





Admittance of Parallel Impedances

$$X_{L1} = 314 \times 31.8 \times 10^{-3} = 10 \, \Omega$$

$$X_{L2} = 314 \times 19.1 \times 10^{-3} = 8 \, \Omega$$

$$X_{C1} = \frac{1}{314 \times 159.24 \times 10^{-9}} = 20 \, \Omega$$
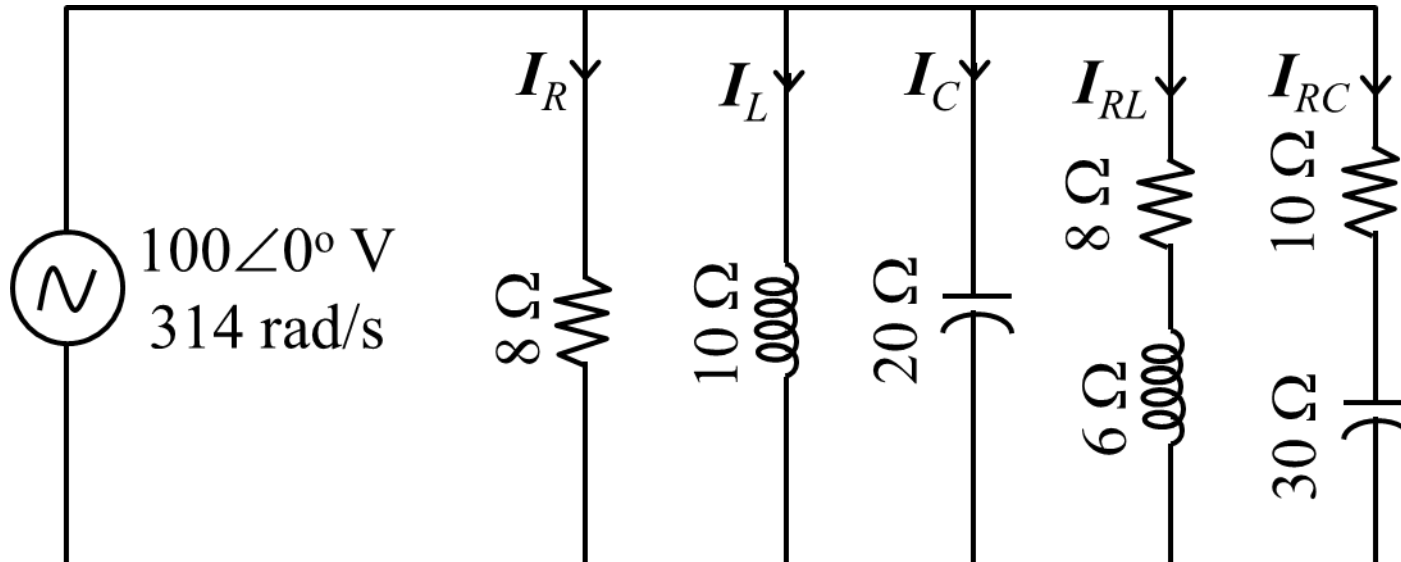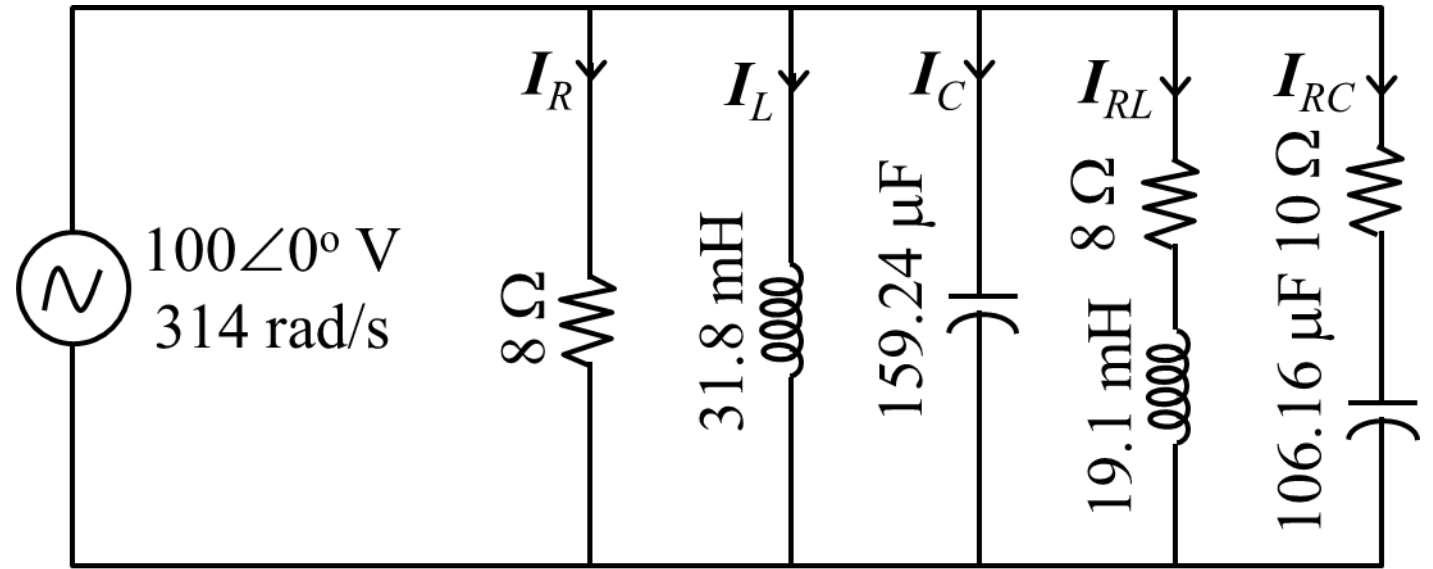
$$X_{C2} = \frac{1}{314 \times 106.16 \times 10^{-9}} = 30 \, \Omega$$



$$Z_R = 8 \Omega$$

$$Y_R = \frac{1}{Z_R} = \frac{1}{8} = 0.125 \text{ S}$$

$$Z_L = j10 \Omega$$

$$Y_L = \frac{1}{Z_L} = \frac{1}{j10} = -j0.1 \text{ S}$$

$$Z_C = -j20 \Omega$$

$$Y_C = \frac{1}{Z_C} = \frac{1}{-j20} = j0.05 \text{ S}$$

$$Z_{RL} = 8 + j6 \Omega$$

$$Y_{RL} = \frac{1}{Z_{RL}} = \frac{1}{8 + j6} = 0.08 - j0.06 \text{ S}$$

$$Z_{RC} = 10 - j30 \Omega$$


$$Y_{RC} = \frac{1}{Z_{RC}} = \frac{1}{10 - j30} = 0.01 + j0.03 \text{ S}$$

$$Y_T = Y_R + Y_L + Y_C + Y_{RL} + Y_{RC}$$

$$Y_T = 0.125 - j0.1 + j0.05 + 0.08 - j0.06 + 0.01 + j0.03$$

$$= 0.215 - j0.08 \text{ S}$$
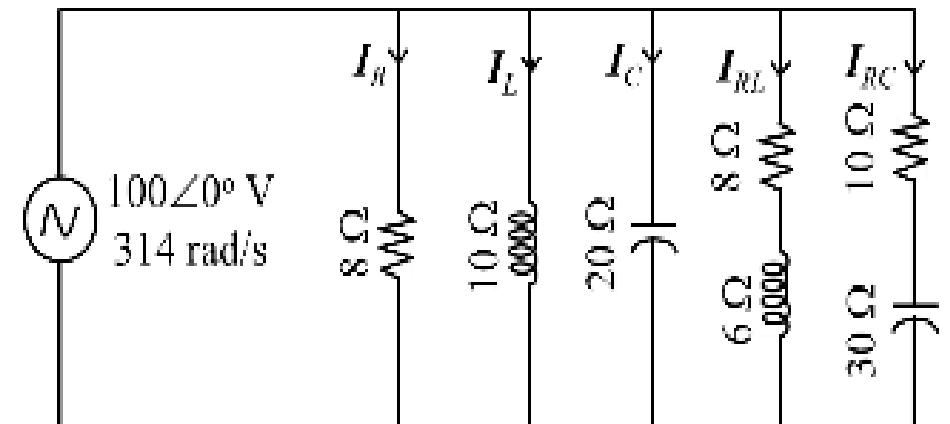
$$Z_T = \frac{1}{Y_T} = \frac{1}{0.215 - j0.08} = 4.086 + j1.52 \Omega$$



$$I_T = VY_T = (100\angle 0^\circ)(0.215 - j0.08) = 21.5 - j8 = 22.94\angle -20.41^\circ \text{ A}$$


$$I_R = VY_R = (100\angle 0^\circ)(0.125) = 12.5 \text{ A}$$

$$I_L = VY_L = (100\angle 0^\circ)(-j0.1) = -j10 = 10\angle -90^\circ \text{ A}$$

$$I_C = VY_C = (100\angle 0^\circ)(j0.05) = j5 = 5\angle 90^\circ \text{ A}$$


$$I_{RL} = VY_{RL} = (100\angle 0^\circ)(0.08 - j0.06) = 8 - j6 \text{ A}$$
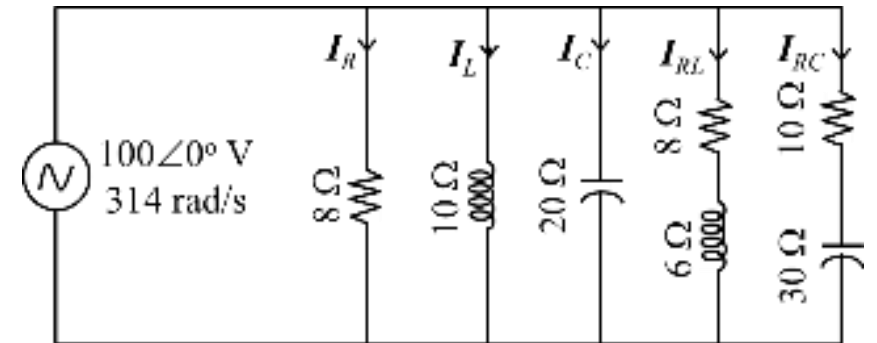
$$I_{RC} = VY_{RC} = (100\angle 0^\circ)(0.01 + j0.03) = 1 + j3 \text{ A}$$




Home Work 5.2

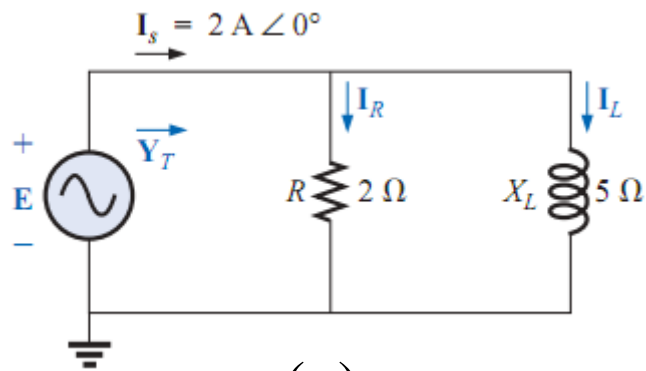
Problem 1: For the following circuits: (i) Find the total admittance. (ii) Draw the admittance diagram. (iii) Find the value of C in microfarads and L in henries. (iv) Find the source voltage (or source current). (v) Find the current of each branch. (vi) Draw the phasor diagram. (vii) Verify Kirchhoff's current law at one node. (viii) Find the average power, reactive power, apparent power, power factor, and reactive factor. (ix) Find the sinusoidal expressions for the currents and voltage. (x) Plot the waveforms for the currents and voltage on the same set of axes.




(a)

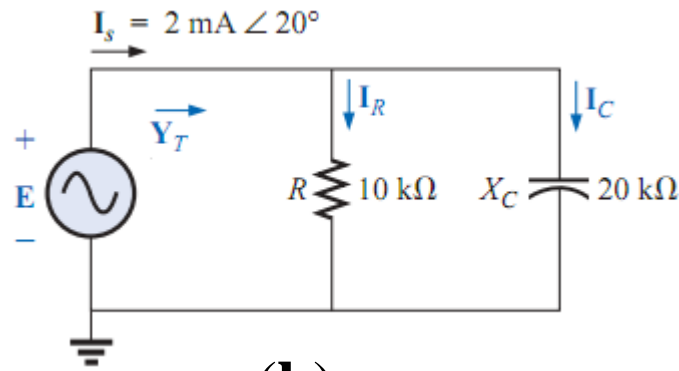

(b)

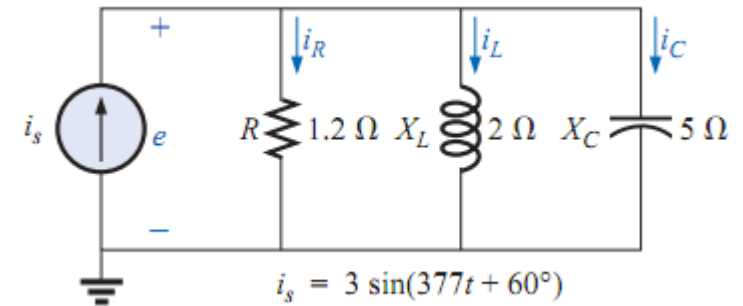


(c)

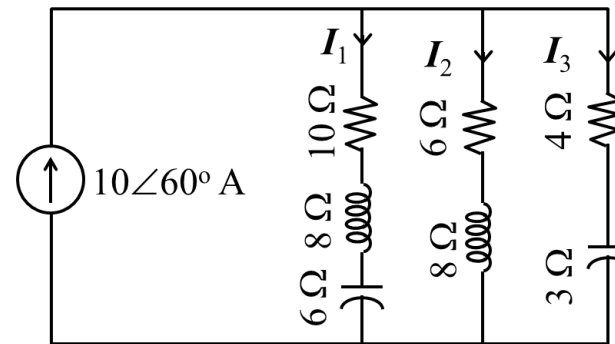

(d)

Home Work 5.3

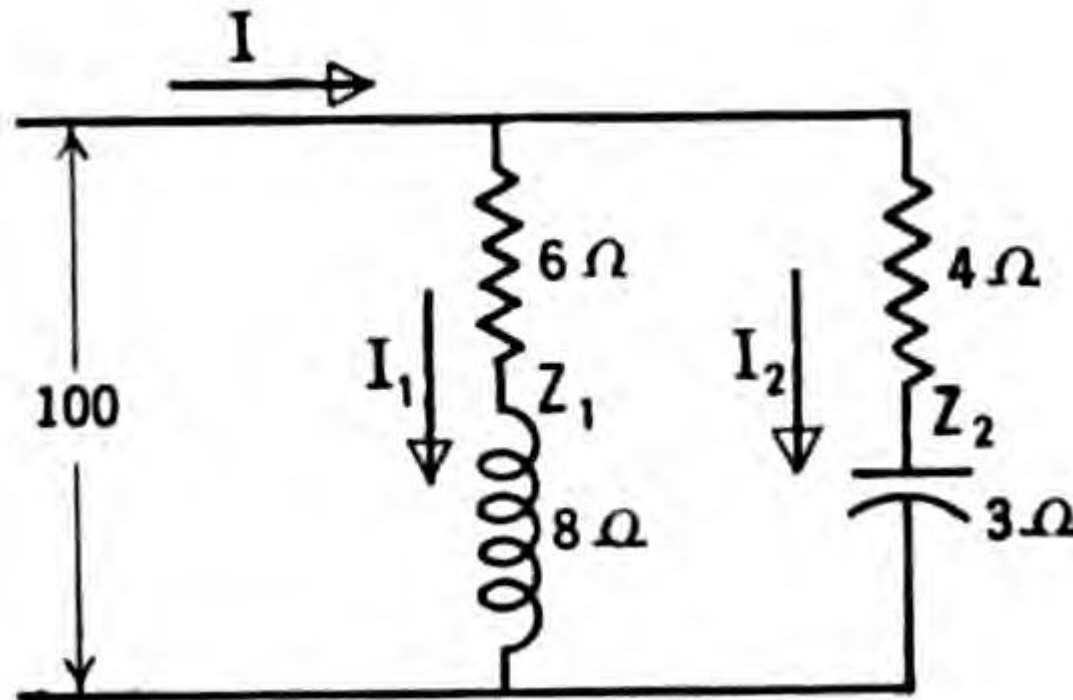Problem 1: For the following circuit diagram (i) find the conductance and susceptance of each branch. (ii) Find the resultant conductance and susceptance. (iii) Find the current I , I_1 , and I_2 . (iv) Draw the vector diagram.



Current Divider Rule

The current (I_x) flows one or more elements in parallel that have total admittance Y_x or impedance Z_x , can be given by:

$$I_x = \frac{Y_x}{Y_T} I = \frac{Z_T}{Z_x} I$$

where, I is the total current flows the parallel circuit, and Y_T is the total admittance of the parallel circuit.

Example

Calculate the current of each branch for the circuit of following figure in phasor form using the current divider rule.

$$Y_R = \frac{1}{8} = 0.125 \text{ S}$$

$$Y_L = \frac{1}{j10} = -j0.1 \text{ S}$$


$$Y_C = \frac{1}{-j20} = j0.05 \text{ S}$$

$$Y_{RL} = \frac{1}{8 + j6} = 0.08 - j0.06 \text{ S}$$

$$Y_{RC} = \frac{1}{10 - j30} = 0.01 + j0.03 \text{ S}$$

$$Y_T = Y_R + Y_L + Y_C + Y_{RL} + Y_{RC}$$
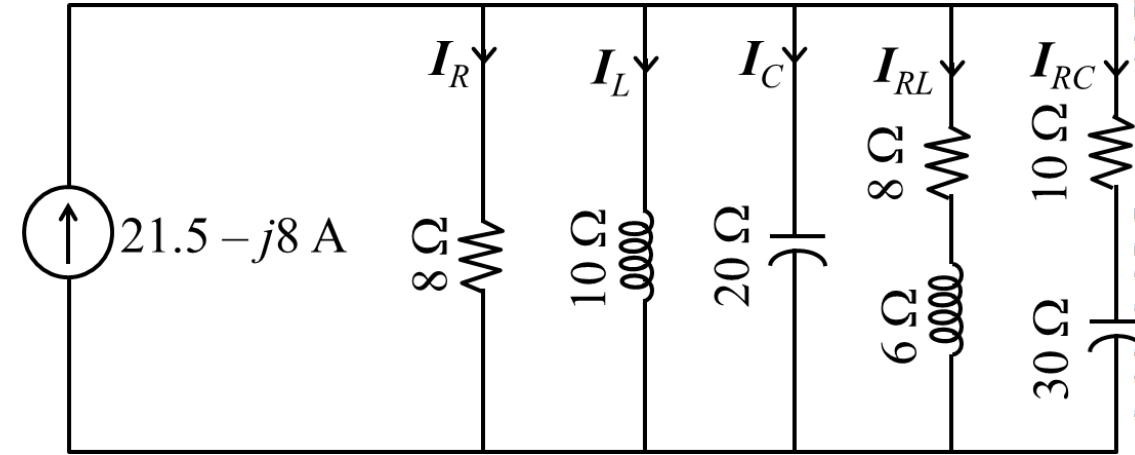
$$Y_T = 0.125 - j0.1 + j0.05 + 0.08 - j0.06 + 0.01 + j0.03 = 0.215 - j0.08 \text{ S}$$



$$Z_T = \frac{1}{Y_T} = \frac{1}{0.215 - j0.08} = 4.086 + j1.52 \Omega$$

$$I_R = \frac{Z_T}{Z_R} I = \frac{Y_R}{Y_T} I = \frac{0.125}{0.215 - j0.08} (21.1 - j8) = 12.5 \text{ A}$$


$$I_L = \frac{Z_T}{Z_L} I = \frac{Y_L}{Y_T} I = \frac{-j0.1}{0.215 - j0.08} (21.1 - j8) = -j10 \text{ A}$$

$$I_C = \frac{Z_T}{Z_C} I = \frac{Y_C}{Y_T} I = \frac{j0.05}{0.215 - j0.08} (21.1 - j8) = j5 \text{ A}$$

$$I_{RL} = \frac{Z_T}{Z_{RL}} I = \frac{Y_{RL}}{Y_T} I = \frac{0.08 - j0.06}{0.215 - j0.08} (21.1 - j8) = 8 - j6 \text{ A}$$

$$I_{RC} = \frac{Z_T}{Z_{RC}} I = \frac{Y_{RC}}{Y_T} I = \frac{0.01 + j0.03}{0.215 - j0.08} (21.1 - j8) = 1 + j3 \text{ A}$$

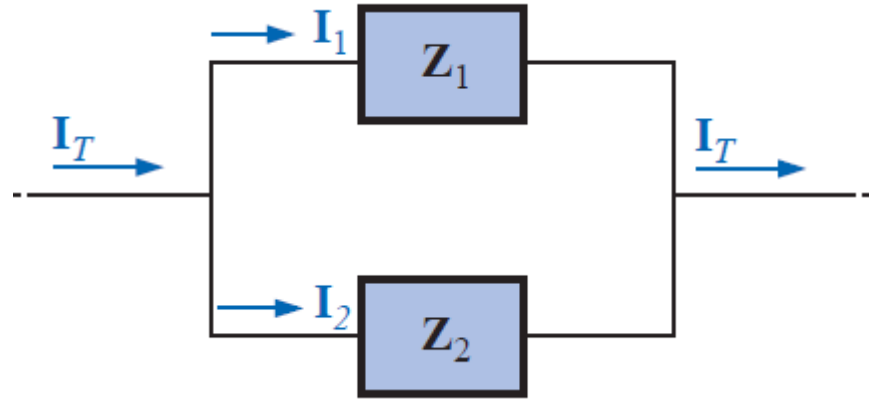Current Divider Rule Only for Two Branch Circuit



$$I_1 = \frac{Y_1}{Y_T} I_T = \frac{Z_T}{Z_1} I_T = \frac{Z_2}{Z_1 + Z_2} I_T$$


$$I_2 = \frac{Y_2}{Y_T} I_T = \frac{Z_T}{Z_2} I_T = \frac{Z_1}{Z_1 + Z_2} I_T$$

Example

Using the current divider rule, find the current through each impedance of following figure.

$$\mathbf{Z}_{RL} = 1 + j8 \ \Omega$$
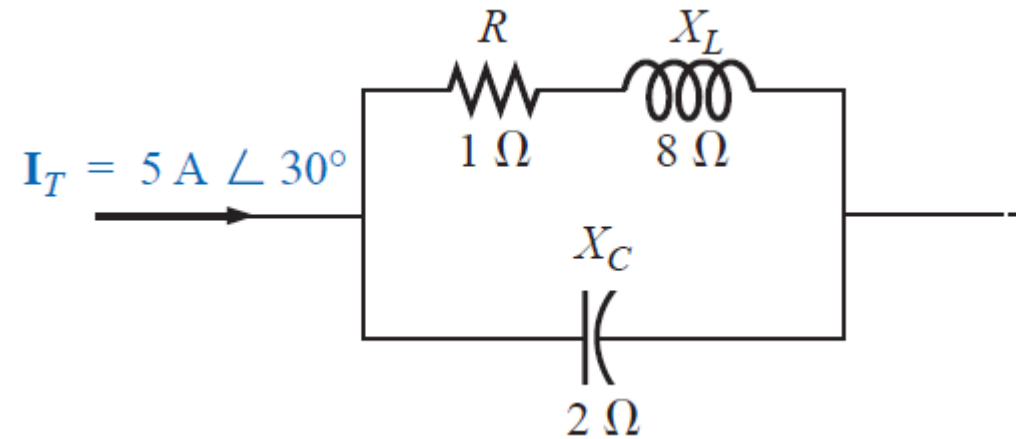
$$\mathbf{Z}_C = -j2 = 2 \angle -90^\circ \ \Omega$$




$$\mathbf{I}_{RL} = \frac{\mathbf{Z}_C}{\mathbf{Z}_{RL} + \mathbf{Z}_C} \mathbf{I}_T = \frac{-j2}{1 + j8 - j2} (5 \angle 30^\circ) = 1.644 \angle -140.54^\circ \text{ A}$$


$$\mathbf{I}_C = \frac{\mathbf{Z}_{RL}}{\mathbf{Z}_{RL} + \mathbf{Z}_C} \mathbf{I}_T = \frac{1 + j8}{1 + j8 - j2} (5 \angle 30^\circ) = 6.625 \angle 32.33^\circ \text{ A}$$

Home Work 5.4

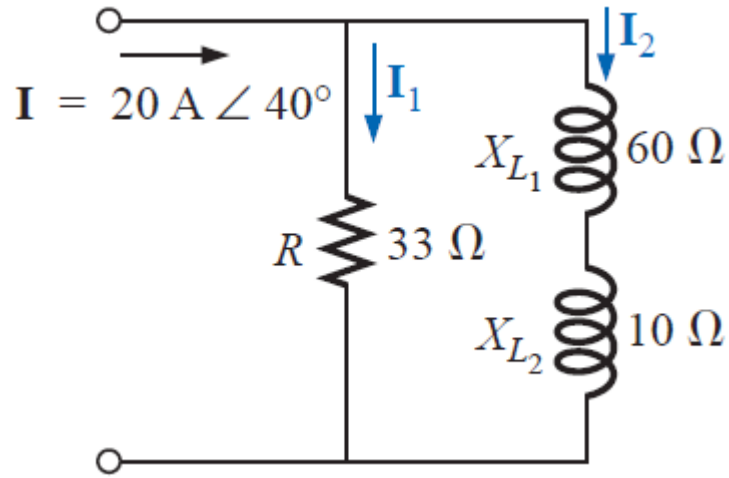
Problem 1: Calculate the current of each branch for the following figure using current divider rule.



(a)


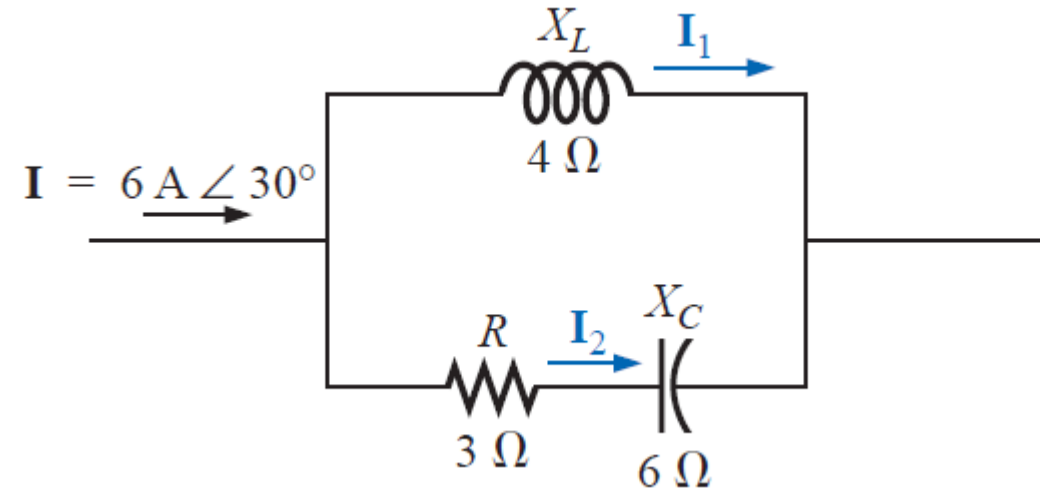


(b)

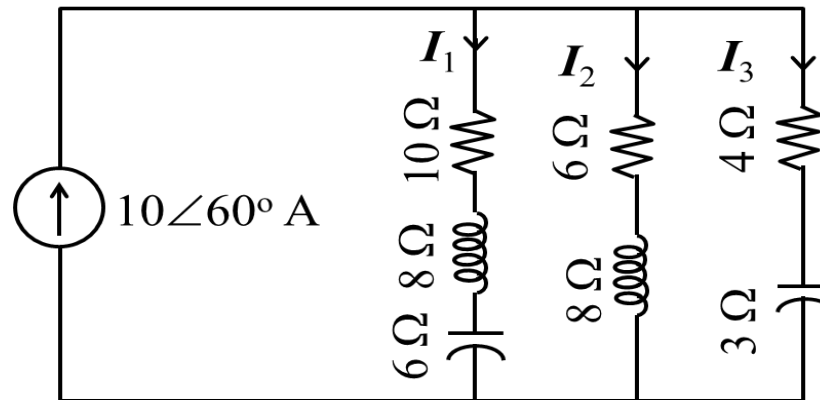


(c)

Series – Parallel Circuit

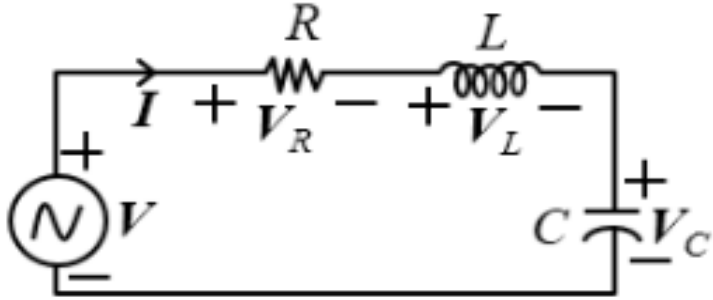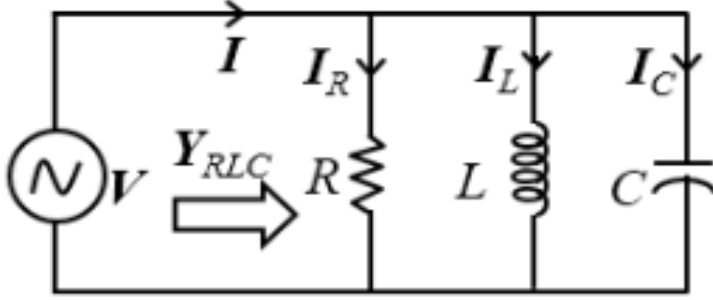RLC Series Circuit	RLC Parallel Circuit
	
$X_L = \omega L; \quad X_C = \frac{1}{\omega C}$	$G = \frac{1}{R}; \quad B_L = \frac{1}{X_L} = \frac{1}{\omega L}; \quad B_C = \frac{1}{X_C} = \omega C$
$Z_R = R; \quad Z_L = jX_L; \quad Z_C = -jX_C$	$Y_R = G; \quad Y_L = -jB_L; \quad Y_C = jB_C$
$Z = \frac{V}{I} = Z_R + Z_L + Z_C = R + jX_L - jX_C$	$Y = \frac{I}{V} = Y_R + Y_L + Y_C = G + jB_C - jB_L$
$I = \frac{V}{Z}; \quad V = IZ$	$I = \frac{V}{Z} = VY; \quad V = IZ = \frac{I}{Y}$
$V_R = IZ_R = \frac{Z_R}{Z}V; \quad V_L = IZ_L = \frac{Z_L}{Z}V$ $V_C = IZ_C = \frac{Z_C}{Z}V$	$I_R = VY_R = \frac{Y_R}{Y}I; \quad I_L = VY_L = \frac{Y_L}{Y}I$ $I_C = VY_C = \frac{Y_C}{Y}I$
$P = I_{rms}^2 R; \quad Q_L = I_{rms}^2 X_L; \quad Q_C = I_{rms}^2 X_C$	$P = I_R^2 R; \quad Q_L = I_L^2 X_L; \quad Q_C = I_C^2 X_C$

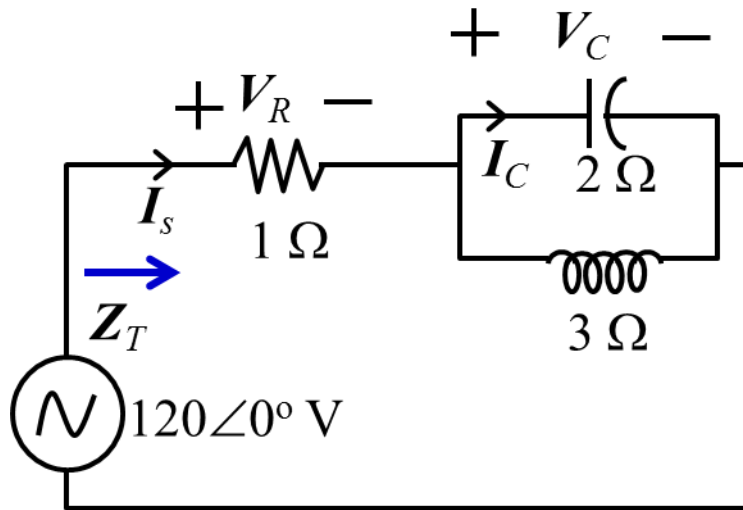Example


For the following circuits: (i) Calculate the total impedance, (ii) Calculate the source current, I_s , and current I_C . (iii) Calculate V_R and V_C . (iv) Compute the power delivered. (v) Find the power factor.



$$Z_1 = 3 \Omega$$

$$Z_2 = \frac{(-j2)(j3)}{-j2 + j3} = -j6 \Omega$$
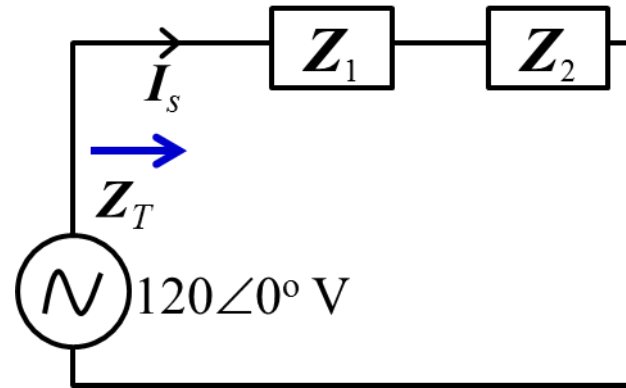
$$\begin{aligned} Z_T &= Z_1 + Z_2 = 3 - j6 \\ &= 6.08 \angle -80.54^\circ \Omega \end{aligned}$$



$$\begin{aligned} I_s &= \frac{V}{Z_T} = \frac{120 \angle 0^\circ}{6.08 \angle -80.54^\circ} \\ &= 19.74 \angle 80.54^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} V_R &= I_s Z_1 = (19.74 \angle 80.54^\circ)(1) \\ &= 19.74 \angle 80.54^\circ \text{ V} \end{aligned}$$

$$V_C = I_s Z_2 = (19.74 \angle 80.54^\circ)(-j6) = 118.44 \angle -9.46^\circ \text{ V}$$

$$I_C = \frac{V_C}{Z_C} = \frac{118.44 \angle -9.46^\circ}{-j2} = 59.22 \angle 80.54^\circ \text{ A}$$

$$P = I_s^2 R = 19.74^2 \times 1 = 389.67 \text{ W}$$

$$pf = \cos \theta = \cos(80.54^\circ) = 0.164 \text{ leading}$$

EXAMPLE 16.2 For the network of Fig. 16.3:

- If \mathbf{I} is $50 \text{ A } \angle 30^\circ$, calculate \mathbf{I}_1 using the current divider rule.
- Repeat part (a) for \mathbf{I}_2 .
- Verify Kirchhoff's current law at one node.



$$\mathbf{Z}_1 = R + jX_L = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ$$

$$\mathbf{Z}_2 = -jX_C = -j8 \Omega = 8 \Omega \angle -90^\circ$$

Using the current divider rule yields

$$\begin{aligned} \mathbf{I}_1 &= \frac{\mathbf{Z}_2 \mathbf{I}}{\mathbf{Z}_2 + \mathbf{Z}_1} = \frac{(8 \Omega \angle -90^\circ)(50 \text{ A } \angle 30^\circ)}{(-j8 \Omega) + (3 \Omega + j4 \Omega)} = \frac{400 \angle -60^\circ}{3 - j4} \\ &= \frac{400 \angle -60^\circ}{5 \angle -53.13^\circ} = \mathbf{80 \text{ A } \angle -6.87^\circ} \end{aligned}$$
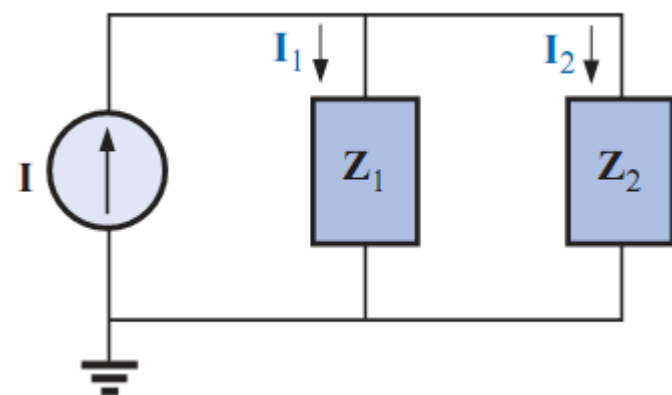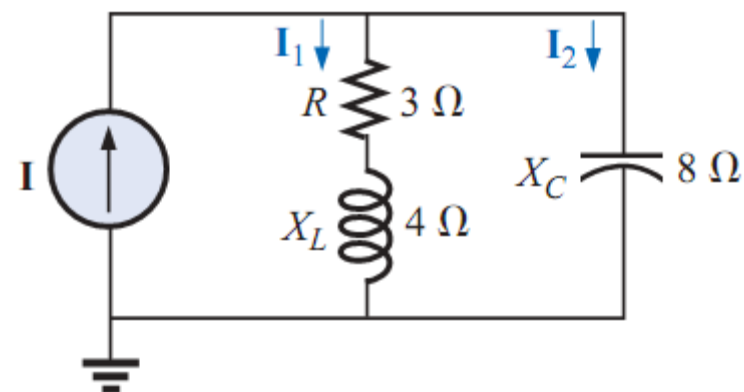
$$\begin{aligned} \mathbf{I}_2 &= \frac{\mathbf{Z}_1 \mathbf{I}}{\mathbf{Z}_2 + \mathbf{Z}_1} = \frac{(5 \Omega \angle 53.13^\circ)(50 \text{ A } \angle 30^\circ)}{5 \Omega \angle -53.13^\circ} = \frac{250 \angle 83.13^\circ}{5 \angle -53.13^\circ} \\ &= \mathbf{50 \text{ A } \angle 136.26^\circ} \end{aligned}$$






$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2$$

$$\begin{aligned} 50 \text{ A } \angle 30^\circ &= 80 \text{ A } \angle -6.87^\circ + 50 \text{ A } \angle 136.26^\circ \\ &= (79.43 - j9.57) + (-36.12 + j34.57) \\ &= 43.31 + j25.0 \\ 50 \text{ A } \angle 30^\circ &= 50 \text{ A } \angle 30^\circ \quad (\text{checks}) \end{aligned}$$

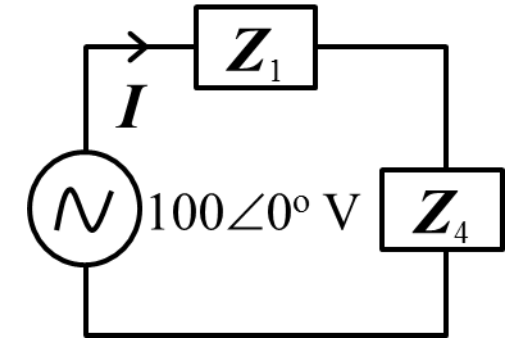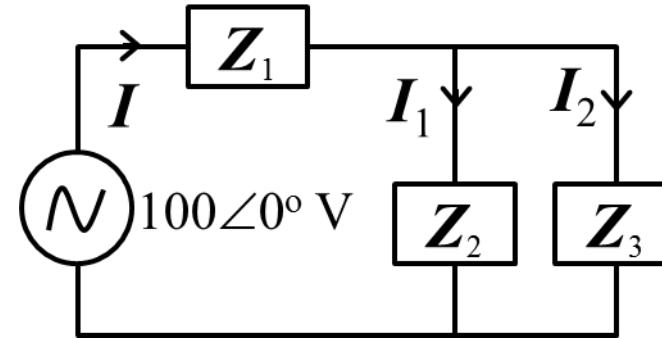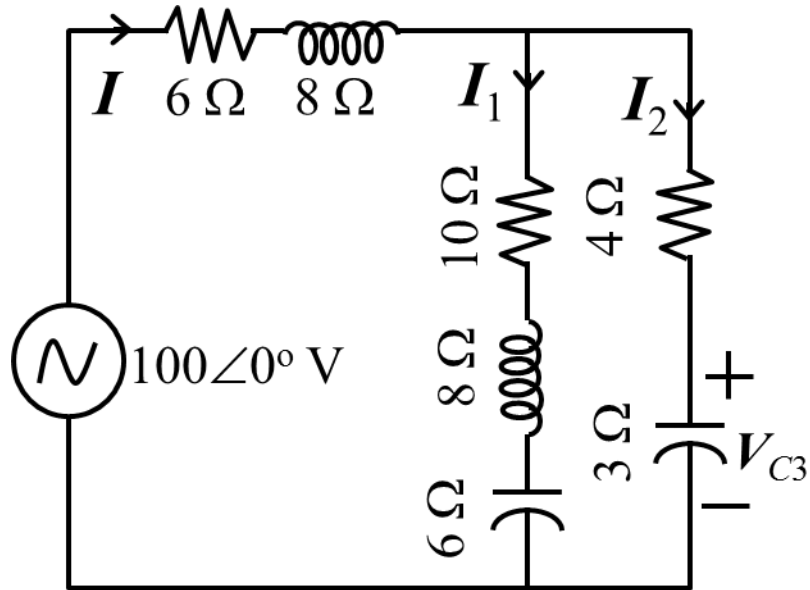Example

For the following circuits: Calculate the total impedance, I , I_1 , I_2 , V_{C3} .



$$Z_4 = \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{(10 + j2)(4 - j3)}{10 + j2 + 4 - j3} = 3.38 - j1.33 \, \Omega$$

$$Z_T = Z_1 + Z_4 = 6 + j8 + 3.38 - j1.33 = 9.38 + j6.67 \, \Omega$$

$$I = \frac{V}{Z_T} = \frac{100 \angle 0^\circ}{9.38 + j6.67} = 7.08 - j5.03 \, \text{A}$$

$$Z_1 = 6 + j8 \, \Omega$$



$$Z_2 = 10 + j8 - j6 = 10 + j2 \, \Omega$$

$$Z_3 = 4 - j3 \, \Omega$$

$$I_1 = \frac{Z_3}{Z_2 + Z_3} I = \frac{4 - j3}{10 + j2 + 4 - j3} (7.08 - j5.03) = 1.15 - j2.87 \text{ A}$$


$$I_2 = \frac{Z_2}{Z_2 + Z_3} I = \frac{10 + j2}{10 + j2 + 4 - j3} (7.08 - j5.03) = 5.9 - j2.16 \text{ A}$$
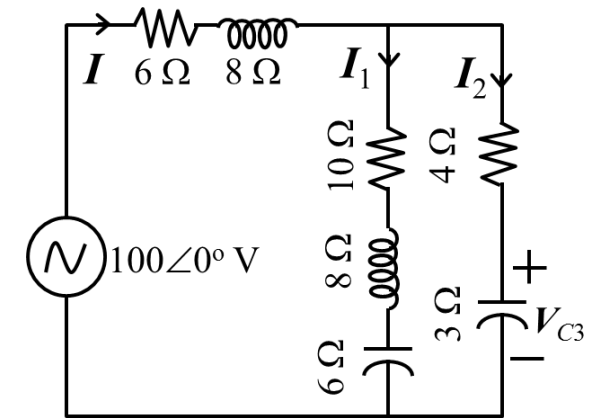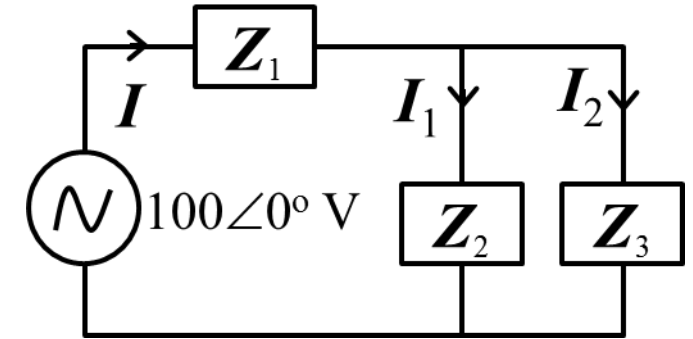
$$V_{C3} = -j3I_2 = -j3(5.9 - j2.16) = -6.48 - j17.8 \text{ A}$$



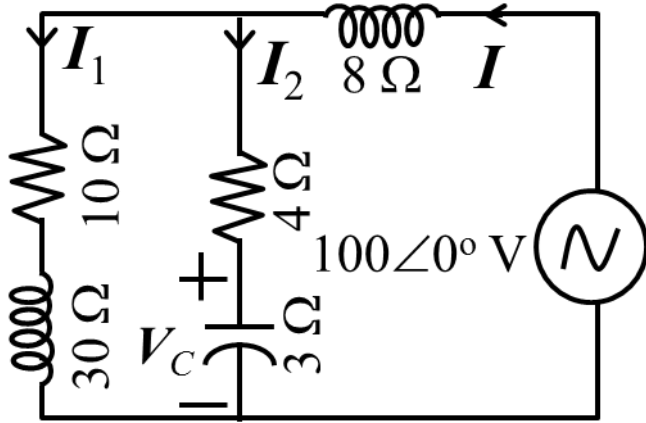Example



For the following circuits: Calculate the total impedance, I , I_1 , I_2 , V_C . Calculate power consumed by load.



$$Z_1 = j8 \, \Omega$$

$$Z_2 = 4 - j3 \, \Omega$$

$$Z_3 = 10 + j30 \, \Omega$$

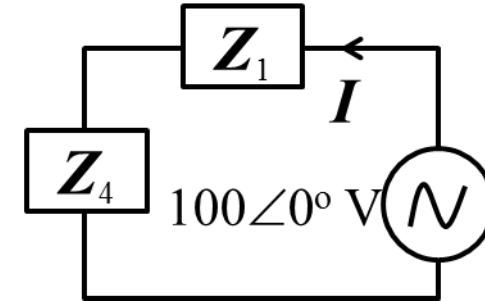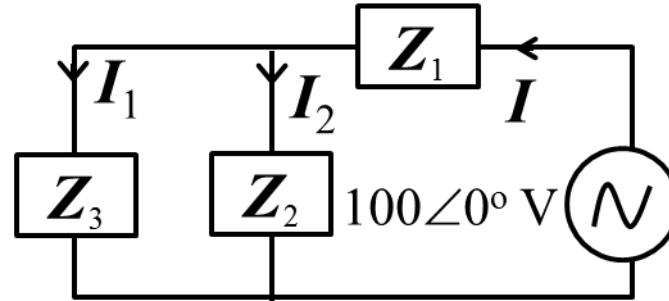

$$Z_4 = \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{(4 - j3)(10 + j30)}{4 - j3 + 10 + j30}$$

$$= 3.84 - j3.84 \, \Omega$$

$$Z_T = Z_1 + Z_4 = j8 + 3.84 - j3.84 = 3.84 + j4.15 \, \Omega$$

$$I = \frac{V}{Z_T} = \frac{100}{3.84 + j4.15} = 12 - j12.96 = 17.66 \angle -47.1^\circ \, \text{A}$$

$$I_1 = \frac{Z_2}{Z_2 + Z_3} I = \frac{4 - j3}{4 - j3 + 10 + j30} (12 - j12.96) = 3.04 \angle -163.77^\circ \text{ A}$$

$$I_2 = \frac{Z_3}{Z_2 + Z_3} I = \frac{10 + j30}{4 - j3 + 10 + j30} (12 - j12.96) = 19.22 \angle -39.07^\circ \text{ A}$$

$$V_C = 3I_2 = 3(19.22 \angle -39.07^\circ) = 57.66 \angle -39.07^\circ \text{ V}$$

$$P = VI \cos \theta = 100 \times 17.66 \cos(-47.1^\circ) = 1200 \text{ W}$$


Power Consumed by Z_2 load. $P_{4\Omega} = I_2^2 \times 4 = 19.22^2 \times 4 = 1107.8 \text{ W}$

Power Consumed by Z_3 load. $P_{10\Omega} = I_1^2 \times 10 = 3.04^2 \times 10 = 92.32 \text{ W}$

$$P = P_{4\Omega} + P_{10\Omega} = 1200 \text{ W}$$

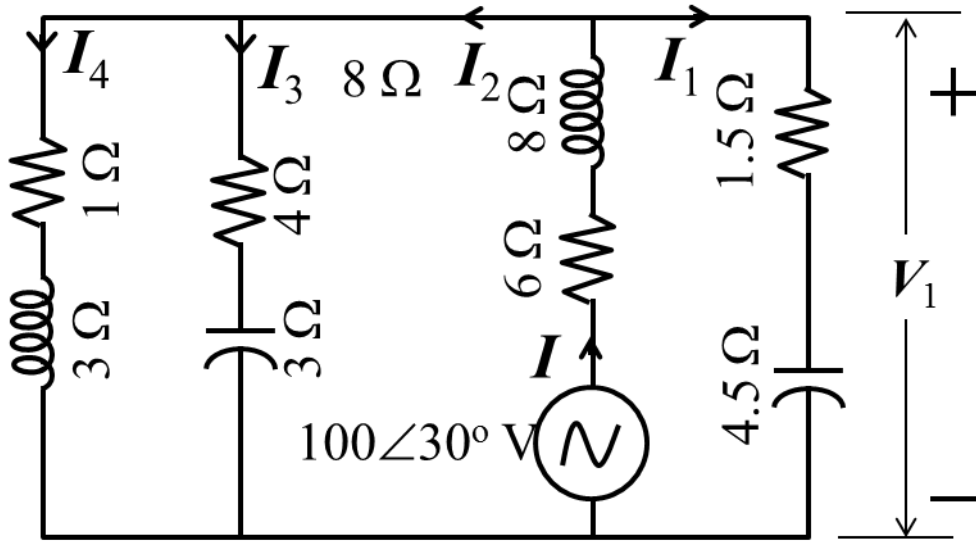Example

For the following circuits: Calculate the total impedance, I , I_1 , I_2 , I_3 , I_4 , V_1 . Calculate power consumed by load.





$$Z_1 = 1.5 - j4.5 = 4.74 \angle -71.6^\circ \Omega$$

$$Z_2 = 6 + j8 = 10 \angle 53.13^\circ \Omega$$

$$Z_3 = 4 - j3 = 5 \angle -36.87^\circ \Omega$$
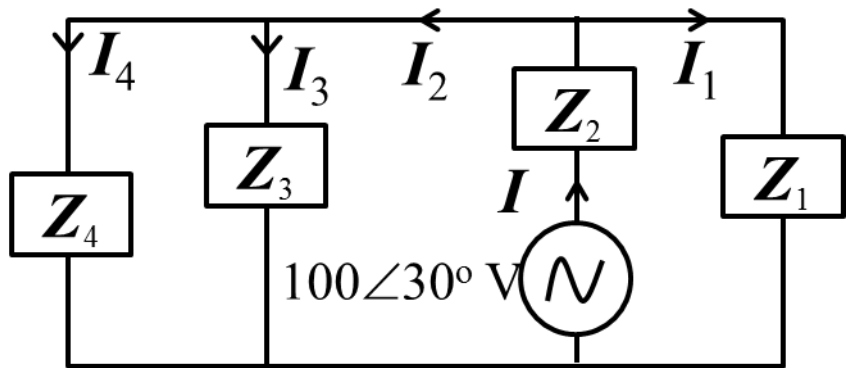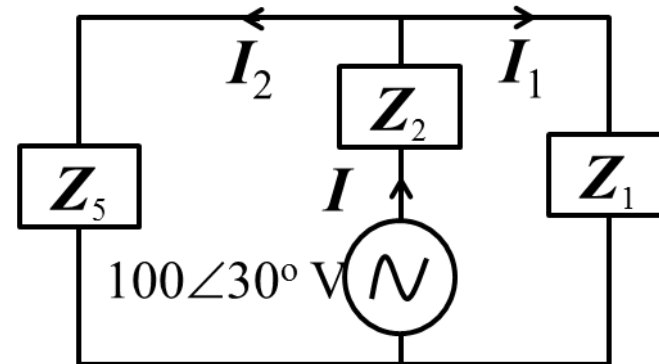
$$Z_4 = 1 + j3 = 3.16 \angle 71.6^\circ \Omega$$



$$Z_5 = \frac{Z_3 Z_4}{Z_3 + Z_4} = \frac{(4 - j3)(1 + j3)}{4 - j3 + 1 + j3} = 2.6 + j1.8 = 3.2 \angle 34.7^\circ \Omega$$




$$\mathbf{Z}_6 = \frac{\mathbf{Z}_5 \mathbf{Z}_1}{\mathbf{Z}_5 + \mathbf{Z}_1} = \frac{(2.6 + j1.8)(1.5 - j4.5)}{2.6 + j1.8 + 1.5 - j4.5} = 3.05 - j0.18 = 3.06 \angle -3.5^\circ \Omega$$

$$\mathbf{Z} = \mathbf{Z}_2 + \mathbf{Z}_6 = 6 + j8 + 3.05 - j0.19 = 9.05 + j7.8 = 11.95 \angle 40.8^\circ \Omega$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{100 \angle 30^\circ}{11.95 \angle 40.8^\circ} = 8.4 \angle -10.8^\circ \text{ A}$$

$$\mathbf{I}_1 = \frac{\mathbf{Z}_5}{\mathbf{Z}_1 + \mathbf{Z}_5} \mathbf{I} = 5.4 \angle 57.3^\circ \text{ A}$$
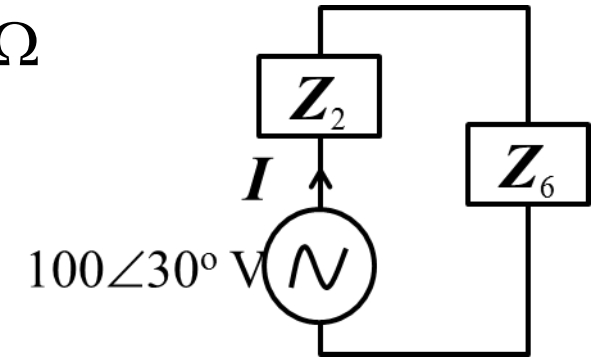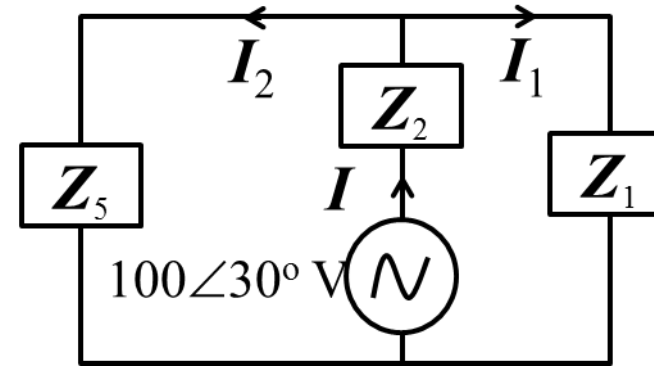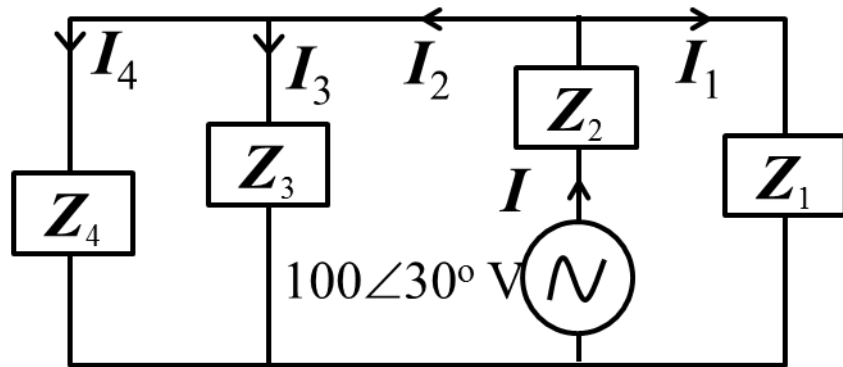
$$\mathbf{I}_2 = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_5} \mathbf{I} = 8.1 \angle -49^\circ \text{ A}$$



$$\mathbf{I}_3 = \frac{\mathbf{Z}_4}{\mathbf{Z}_3 + \mathbf{Z}_4} \mathbf{I}_2 = 5.1 \angle 22^\circ \text{ A}$$

$$\mathbf{I}_4 = \frac{\mathbf{Z}_3}{\mathbf{Z}_3 + \mathbf{Z}_4} \mathbf{I}_2 = 8.1 \angle -85.87^\circ \text{ A}$$

$$\mathbf{V}_1 = \mathbf{Z}_1 \mathbf{I}_1 = 25.5 \angle -14.3^\circ \text{ V}$$

$$P_{1\Omega} = I_4^2 \times 1 = 8.1^2 \times 1 = 65.312 \text{ W}$$

$$P_{4\Omega} = I_3^2 \times 4 = 5.1^2 \times 4 = 104.5 \text{ W}$$

$$P_{6\Omega} = I^2 \times 6 = 5.4^2 \times 6 = 419.74 \text{ W}$$

$$P_{1.5\Omega} = I_1^2 \times 1.5 = 5.4^2 \times 1.5 = 43.54 \text{ W}$$

$$P = P_{1\Omega} + P_{4\Omega} + P_{8\Omega} + P_{1.5\Omega} = 633.1 \text{ W}$$

$$\theta_v = 30^\circ$$

$$\theta_i = -10.8^\circ$$

$$\theta = \theta_v - \theta_i = 40.8^\circ$$

$$pf = \cos \theta = \cos(40.8^\circ) = 0.76$$

$$rf = \sin \theta = \sin(40.8^\circ) = 0.65$$

$$Q_{3L} = I_4^2 \times 3 = 8.1^2 \times 3 = 195.94 \text{ Var}$$

$$Q_{3C} = -I_3^2 \times 3 = 5.1^2 \times 3 = -78.37 \text{ Var}$$

$$Q_{8L} = I^2 \times 8 = 8.36^2 \times 3 = 559.65 \text{ Var}$$

$$Q_{4.5C} = -I_1^2 \times 4.5 = 5.4^2 \times 4.5 = -130.62 \text{ Var}$$




$$Q = Q_{3L} + Q_{3C} + Q_{8L} + Q_{4.5C} = 546.58 \text{ Var}$$

$$P = 100 \times 8.36 \times \cos(40.8^\circ) = 633.1 \text{ W}$$

$$Q = 100 \times 8.36 \times \sin(40.8^\circ) = 546.58 \text{ Var}$$

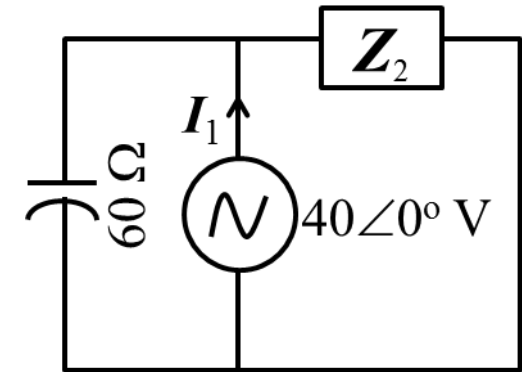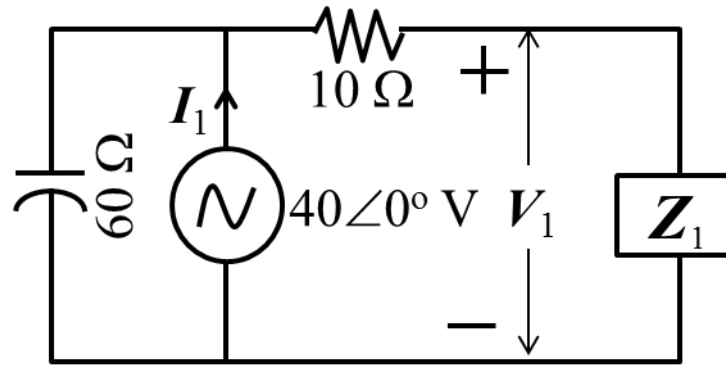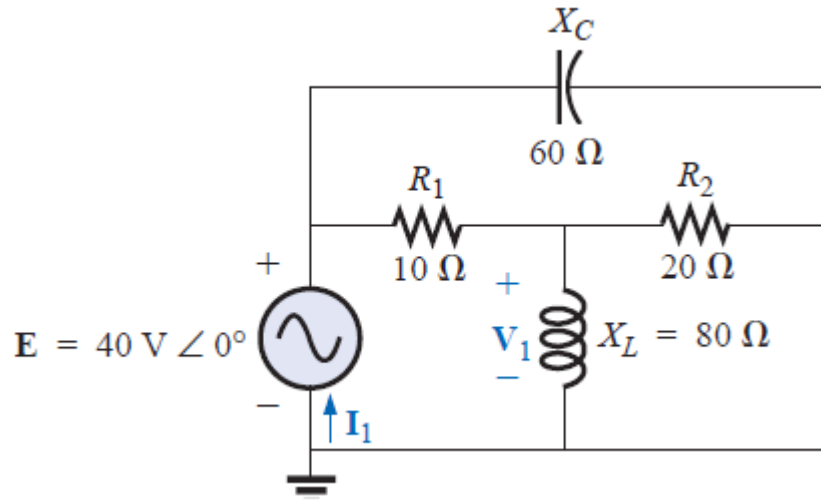Example

For the following circuits: Calculate the total impedance, I_1 , V_1 .



$$Z_1 = \frac{1}{\frac{1}{20} + \frac{1}{j80}} = 18.82 + j4.7 = 19.4 \angle 14^\circ \Omega$$

$$Z_2 = 10 + Z_1 = 28.82 + j4.7 = 29.2 \angle 9.27^\circ \Omega$$



$$Z = \frac{-j60 \times Z_2}{-j60 + Z_2} = 26.7 - j8.8 = 28.1 \angle -18.3^\circ \Omega$$

$$I = \frac{V}{Z} = 1.35 + j0.446 = 1.42 \angle 18.3^\circ \text{ A}$$

$$V_1 = \frac{Z_1}{10 + Z_1} V = 26.48 + j2.2 = 26.57 \angle 4.8^\circ \text{ V}$$



Home Work 5.5

Problem 1: Calculate Z_T , V_2 , I_L for the following network. Also calculate the power factor, reactive factor, power, reactive power and apparent power.

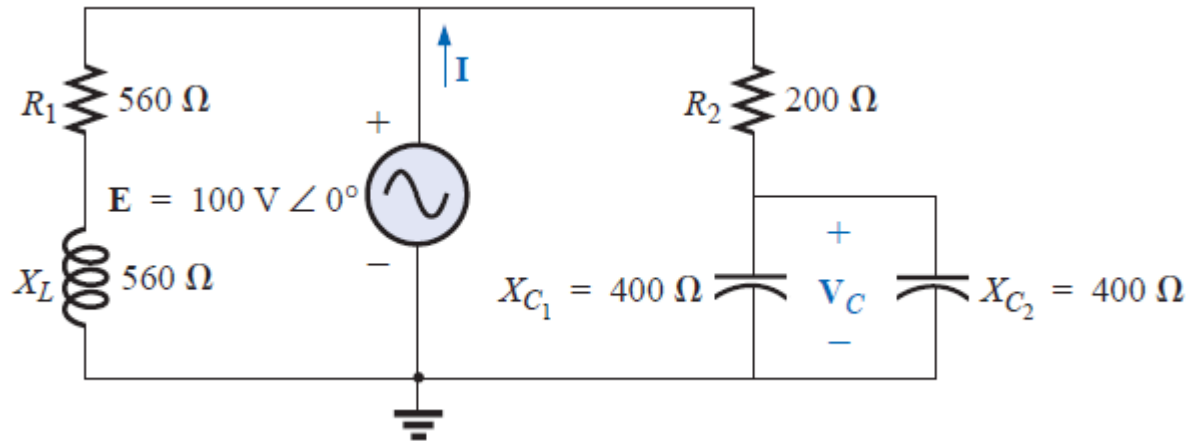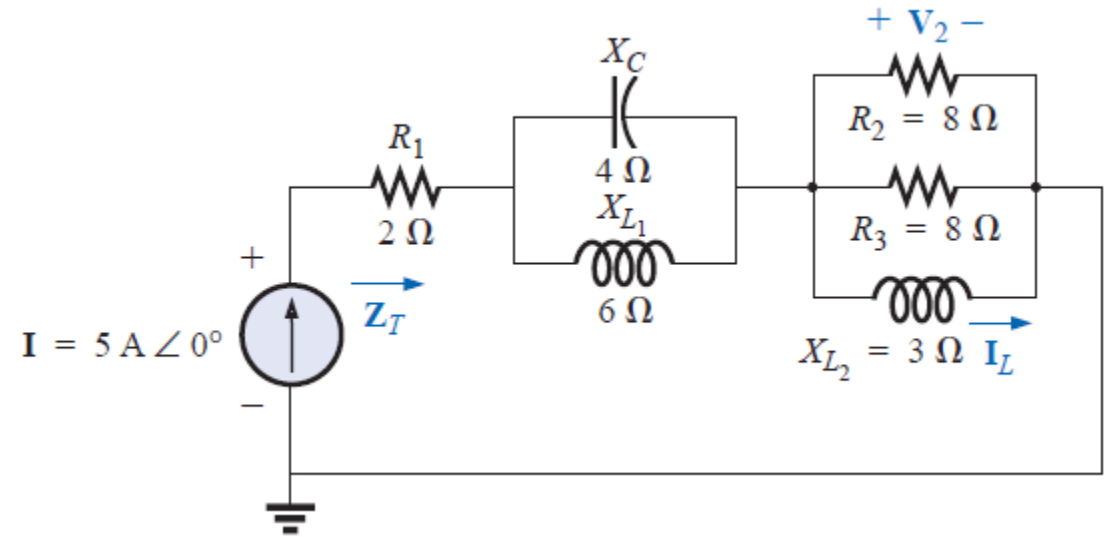

Problem 2: Calculate I , and V_C for the following network. Also calculate the power factor, reactive factor, power, reactive power and apparent power.

Problem 3: Calculate I_1 , V_C , V_{ab} for the following network.

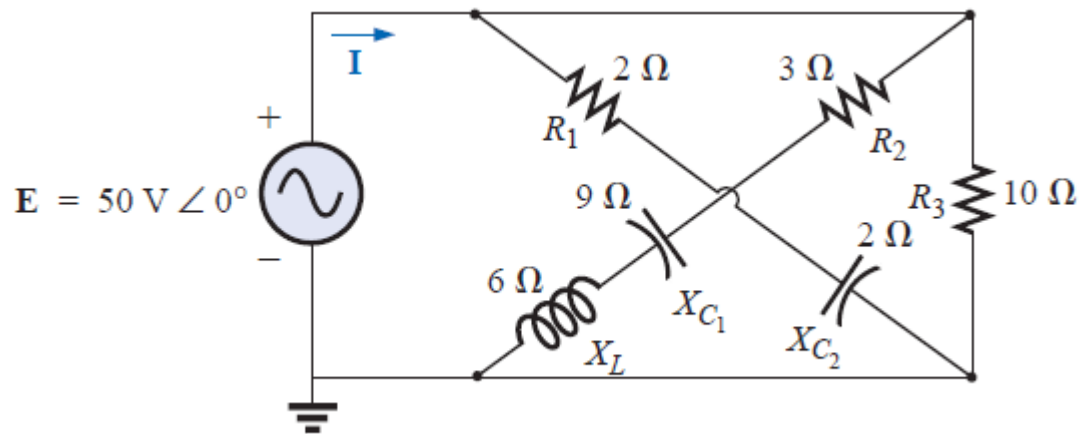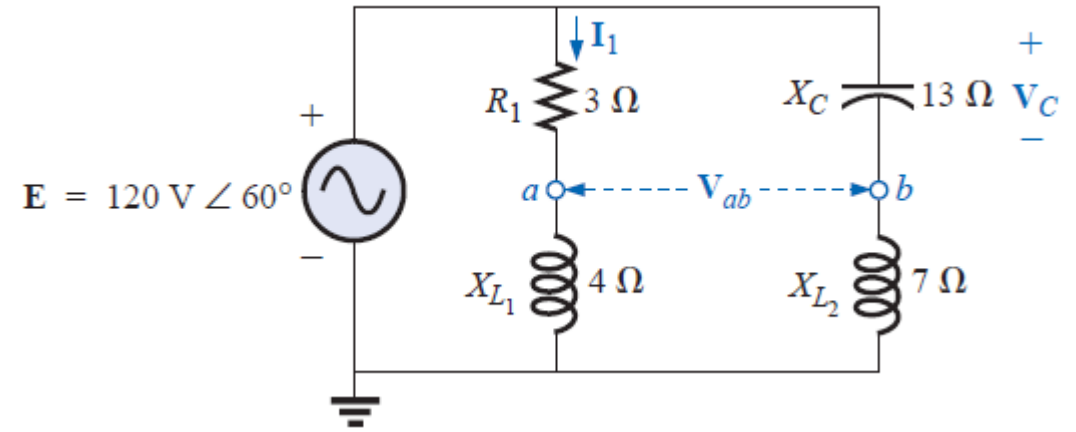

Problem 4: Calculate I for the following network. Also calculate the power factor, reactive factor, power, reactive power and apparent power.